

EE288 – HW6 Report

1 stage of a 1.5 bit/stage Pipeline ADC

(using 45nm CMOS Technology)

Muhammad Aldacher

Student ID: 011510317

Overview

1. Comparator Circuit
2. Bootstrap & CMOS switches
3. Sub-ADC Logic Circuit
4. Whole System simulations
 - a) Normal Mode
 - b) 2x Gain Mode
5. VerilogA Blocks


(1)

Comparator

[illegible]


Size of the NMOS & PMOS of the TGs here (m) = 3

PreAmp

 

Device	Size (in terms of fingers, m)
M1, M2	5
M3, M4, M5, M6	1
Mc	2
Mcx	1
Ideal Current Source	8.8 μ A


Regenerative Latch

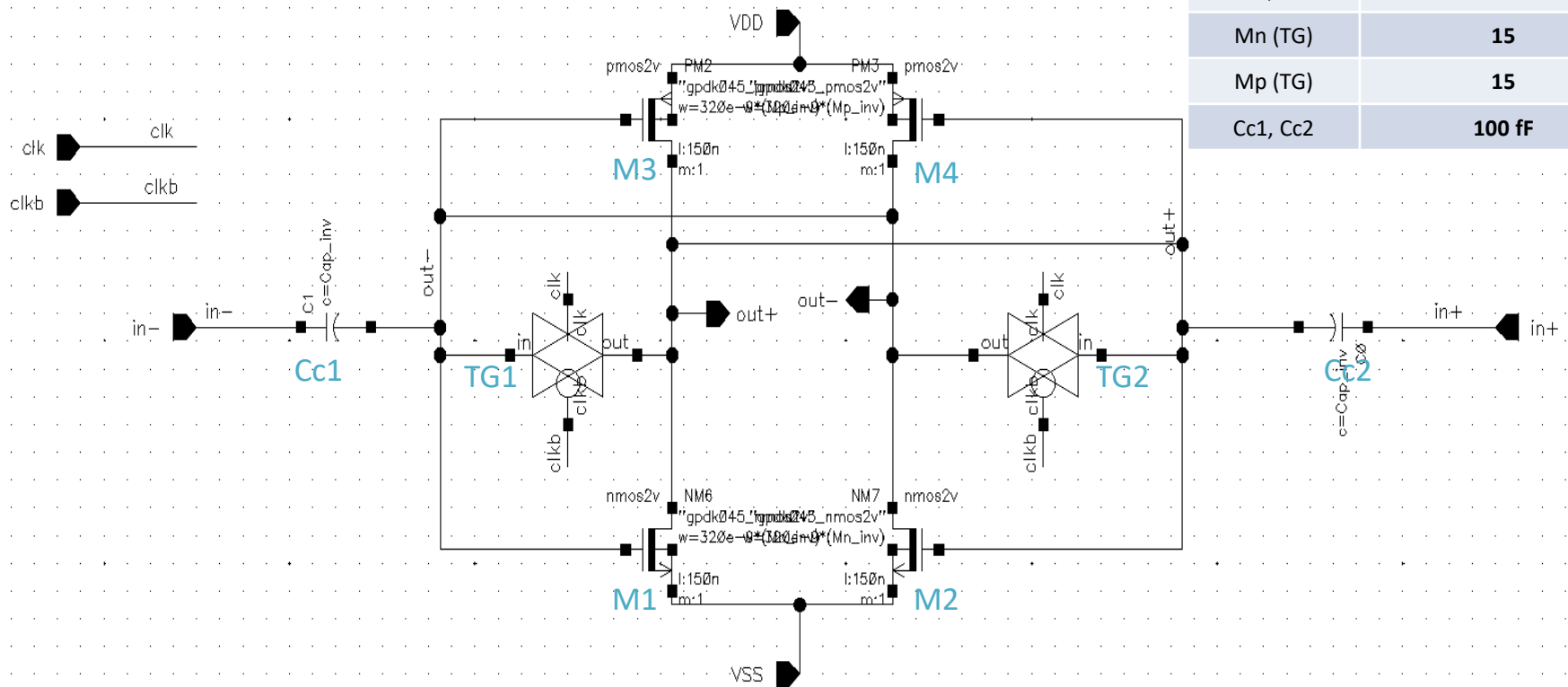

Device	Size (in terms of fingers, m)
M1, M2	5
M3, M4	10
Mn (TG)	15
Mp (TG)	15
Cc1, Cc2	100 fF

RS Latch

Device	Size (in terms of fingers, m)
M1, M2	2
M3, M4	1
M5, M6	10
M7, M8	5
M9, M10	10

 

Overdrive test Waveforms

Diff Vin_min = 2 x 0.5 mV
(Smallest Resolution)

Transient Response


Sat Apr 7 23:32:40 2018



(2)

Switches Circuits


Bootstrap Switch

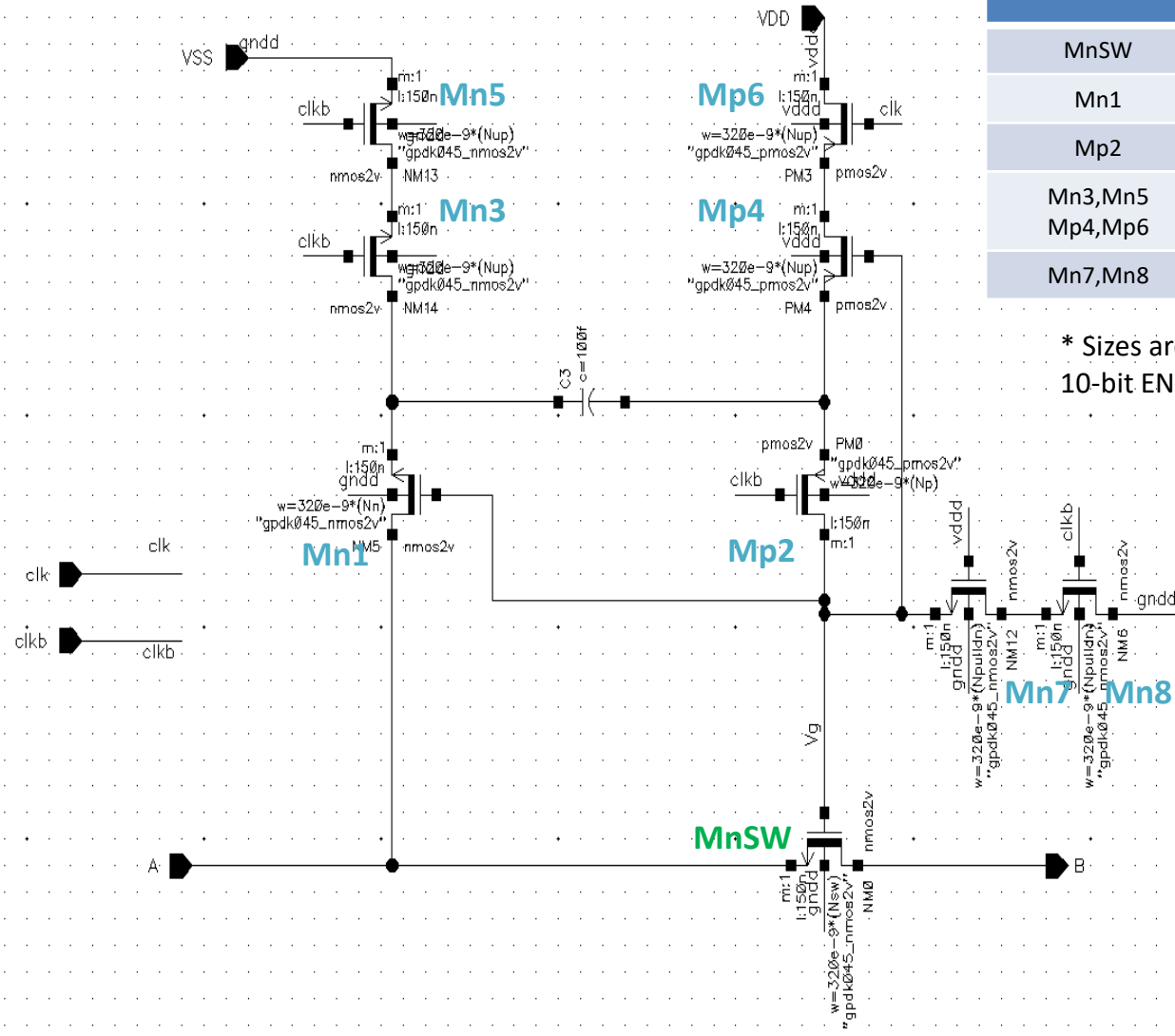

Device	Size (in terms of fingers, m)
MnSW	30
Mn1	20
Mp2	1
Mn3,Mn5 Mp4,Mp6	1
Mn7,Mn8	28

* Sizes are chosen to give a 10-bit ENOB for a 1pF load

CMOS Transmission Gate Switch

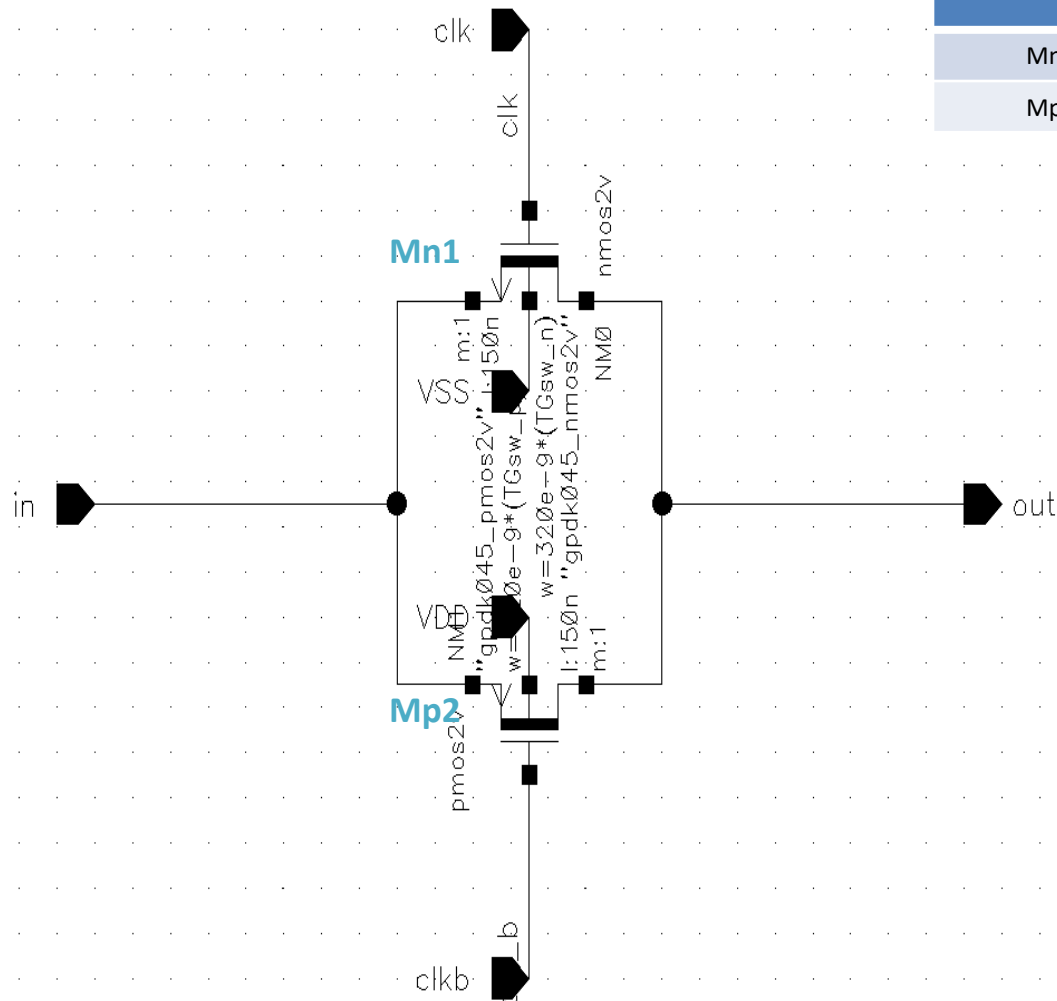


Device	Size (in terms of fingers, m)
Mn1	7
Mp2	7

(3)


Sub-ADC Logic Circuit

Whole Logic Circuit

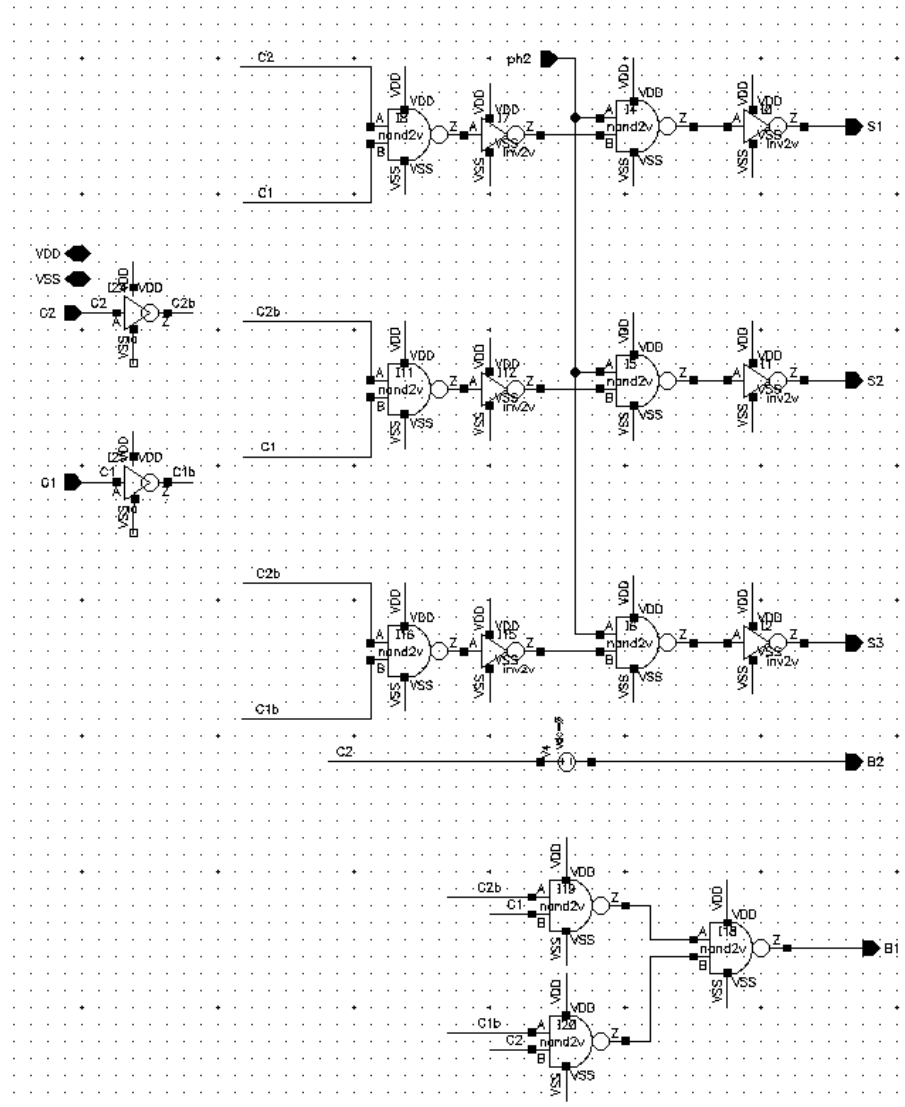


Logic Circuits used

NAND Gate Circuit

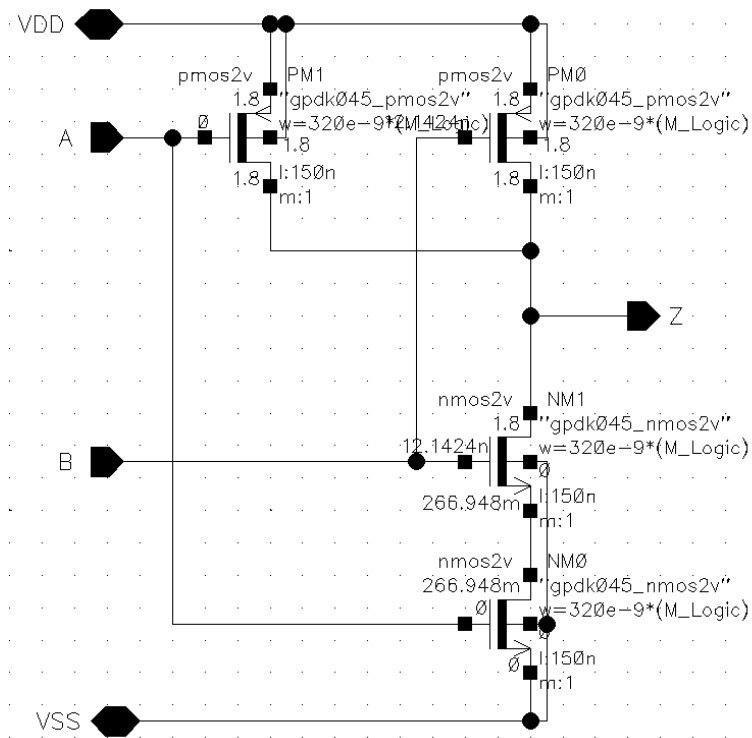


Inverter Circuit

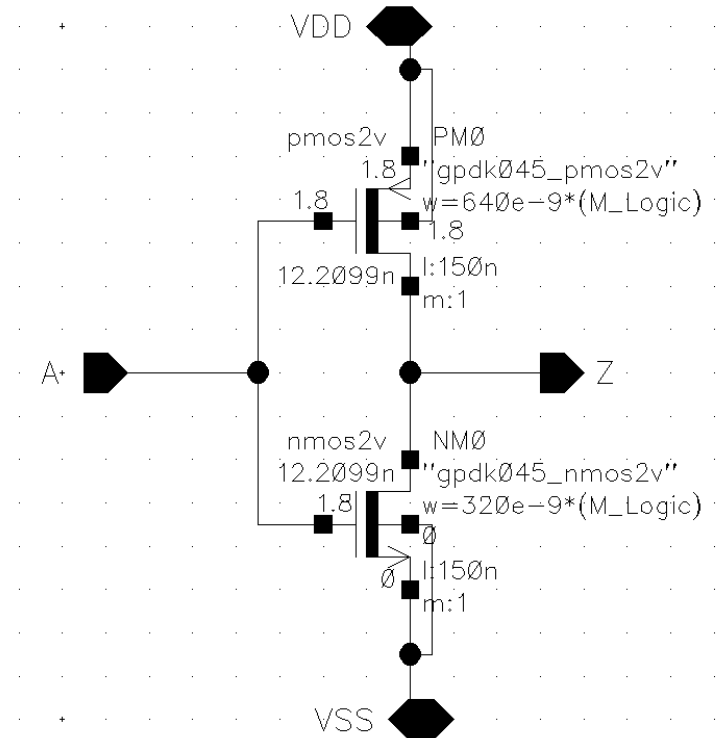


(4)

Whole System

Testbench

 

Simulation Setup

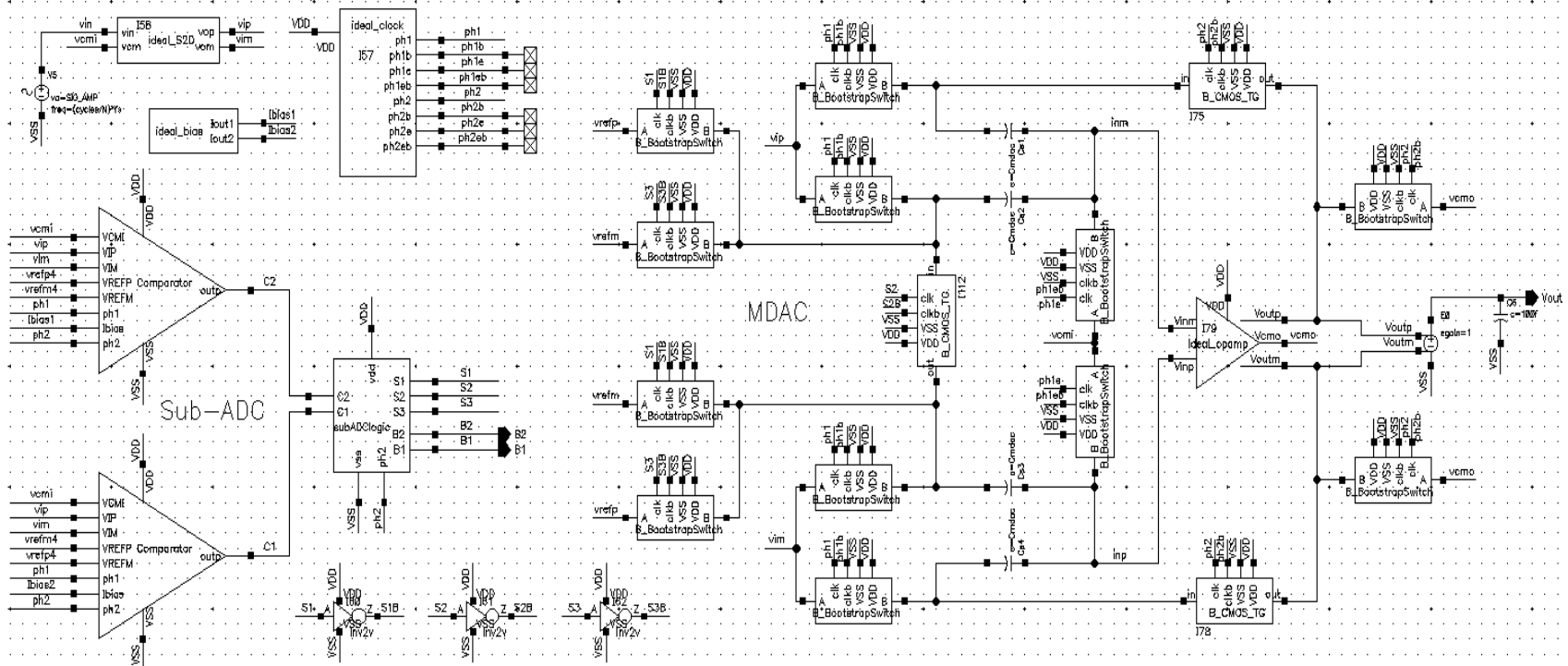

During ph1, input is sampled into subADC and MDAC. During ph2, subADC makes decision on S1-3 position and opamp provides Vout as follows:

If C2 C1 = 11, B2 B1 = 10, S1=1, $V_{out} = 2V_{in} - V_{fs}$
 If C2 C1 = 01, B2 B1 = 01, S2=1, $V_{out} = 2V_{in} - 0$
 If C2 C1 = 00, B2 B1 = 00, S3=1, $V_{out} = 2V_{in} + V_{fs}$

Simulation Results


(a) Normal Mode

Simulation Results

1- Normal Mode

Transient Response

Fri May 4 00:07:15 2018

 


Simulation Results

1- Normal Mode

1) If $V_{in} < V_{refm} \rightarrow V_{out} = 2 \cdot V_{in} + V_{fs}$

Transient Response

Fri May 4 00:32:57 2018

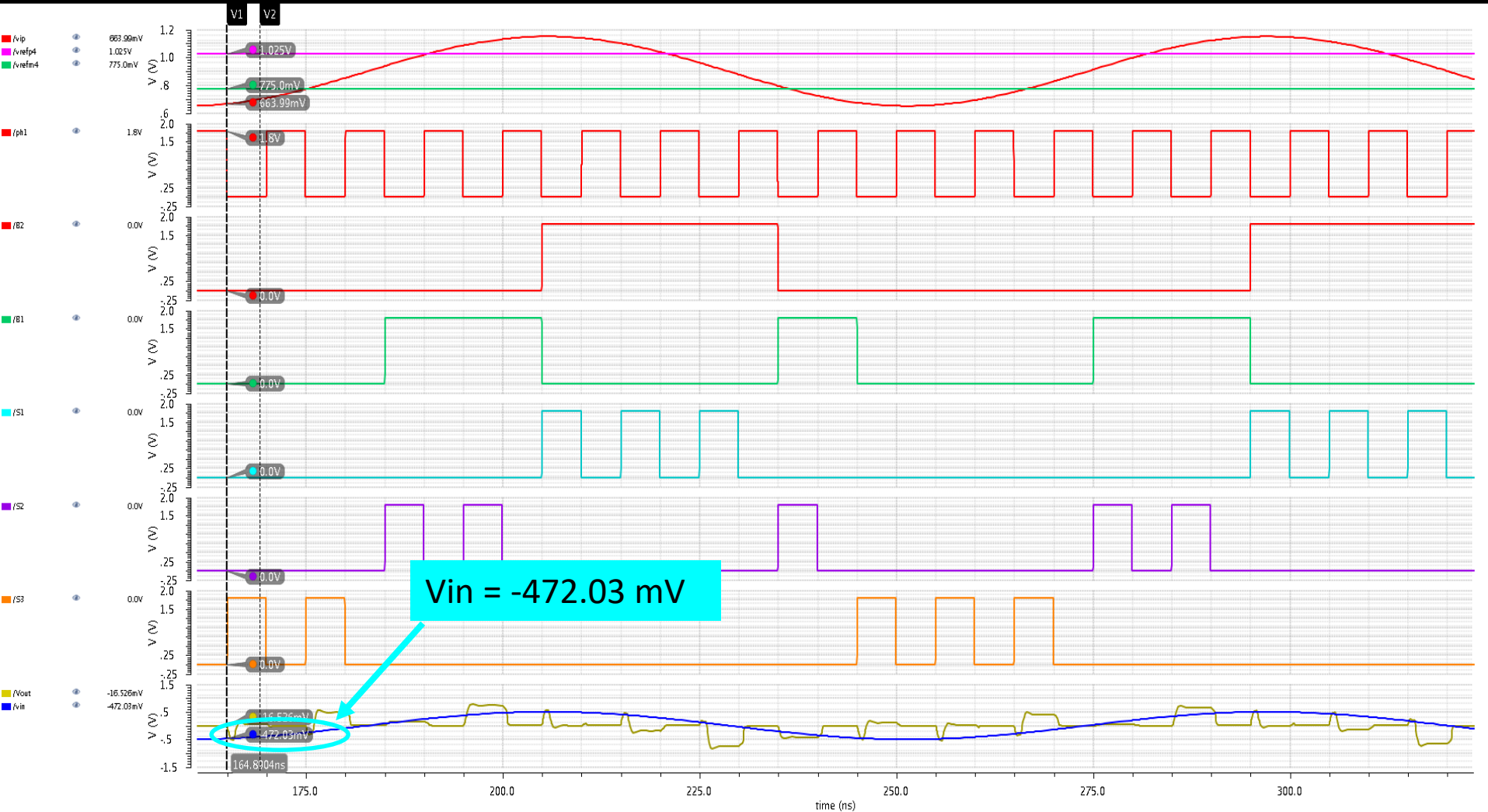


Simulation Results

1- Normal Mode

1) If $V_{in} < V_{refm}$ $\rightarrow V_{out} = 2 \cdot V_{in} + V_{fs}$

Transient Response

Fri May 4 00:32:57 2018

 


Simulation Results

1- Normal Mode

2) If $V_{refm} < V_{in} < V_{refp} \rightarrow V_{out} = 2 * V_{in}$

Transient Response

Fri May 4 00:32:57 2018

 


Simulation Results

1- Normal Mode

2) If $V_{refm} < V_{in} < V_{refp} \rightarrow V_{out} = 2 * V_{in}$

Transient Response

Fri May 4 00:32:57 2018

 


Simulation Results

1- Normal Mode

3) If $V_{in} > V_{refp} \rightarrow V_{out} = 2 * V_{in} - V_{fs}$

Transient Response

Fri May 4 00:32:57 2018

 


Simulation Results

1- Normal Mode

3) If $V_{in} > V_{refp}$ → $V_{out} = 2 * V_{in} - V_{fs}$

Transient Response

Fri May 4 00:32:57 2018

 

Simulation Results


(b) 2x Gain Mode

Simulation Results

2- 2x Gain Mode (Signal input Amp = 0.5v)

Transient Response

Thu May 3 20:53:08 2018

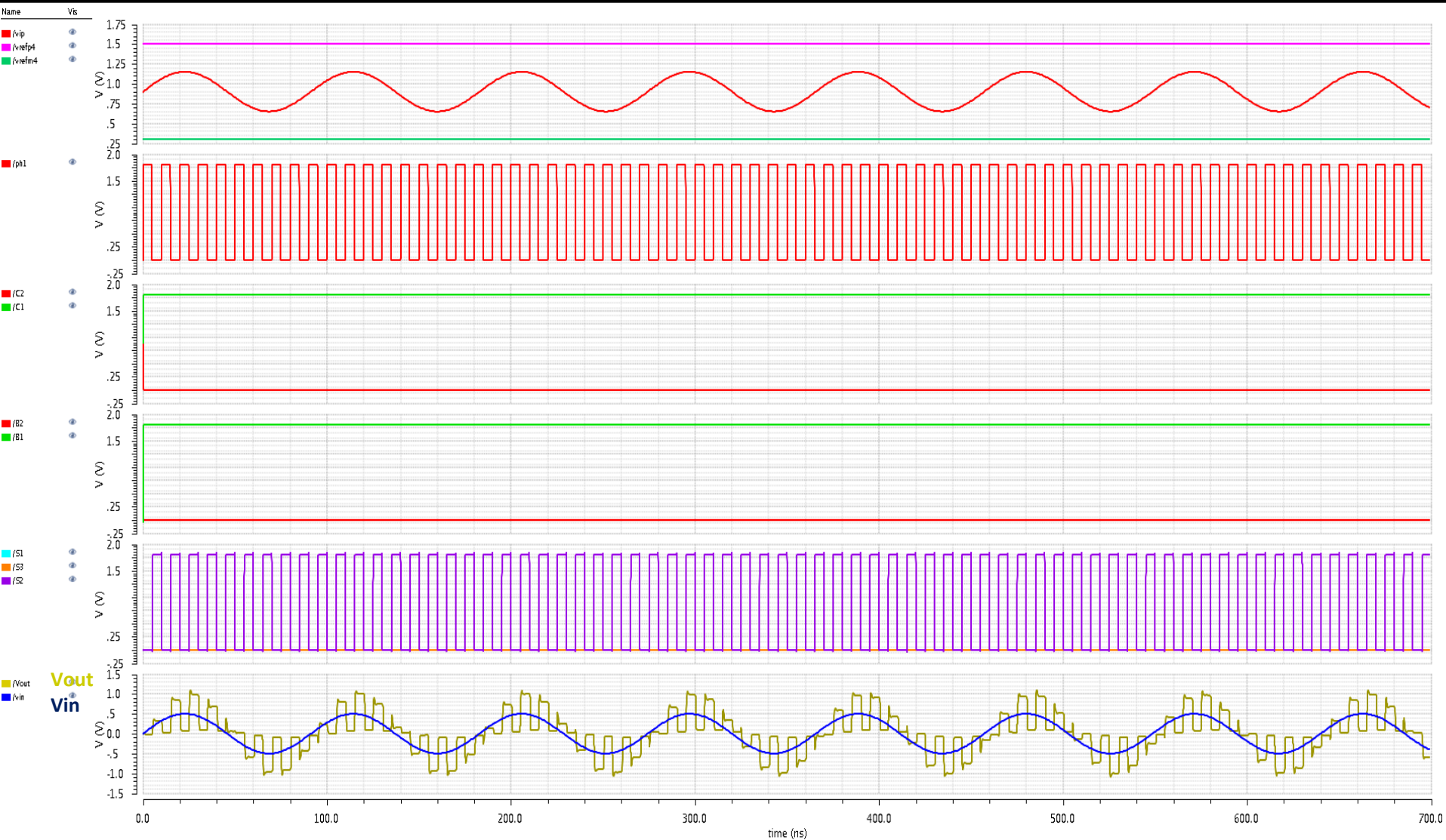


Simulation Results

2- 2x Gain Mode (Signal input Amp = 0.5v)

Transient Response

Thu May 3 20:53:08 2018

 


Simulation Results

2- 2x Gain Mode (Signal input Amp = 0.5v)

Transient Response

Thu May 3 20:53:08 2018

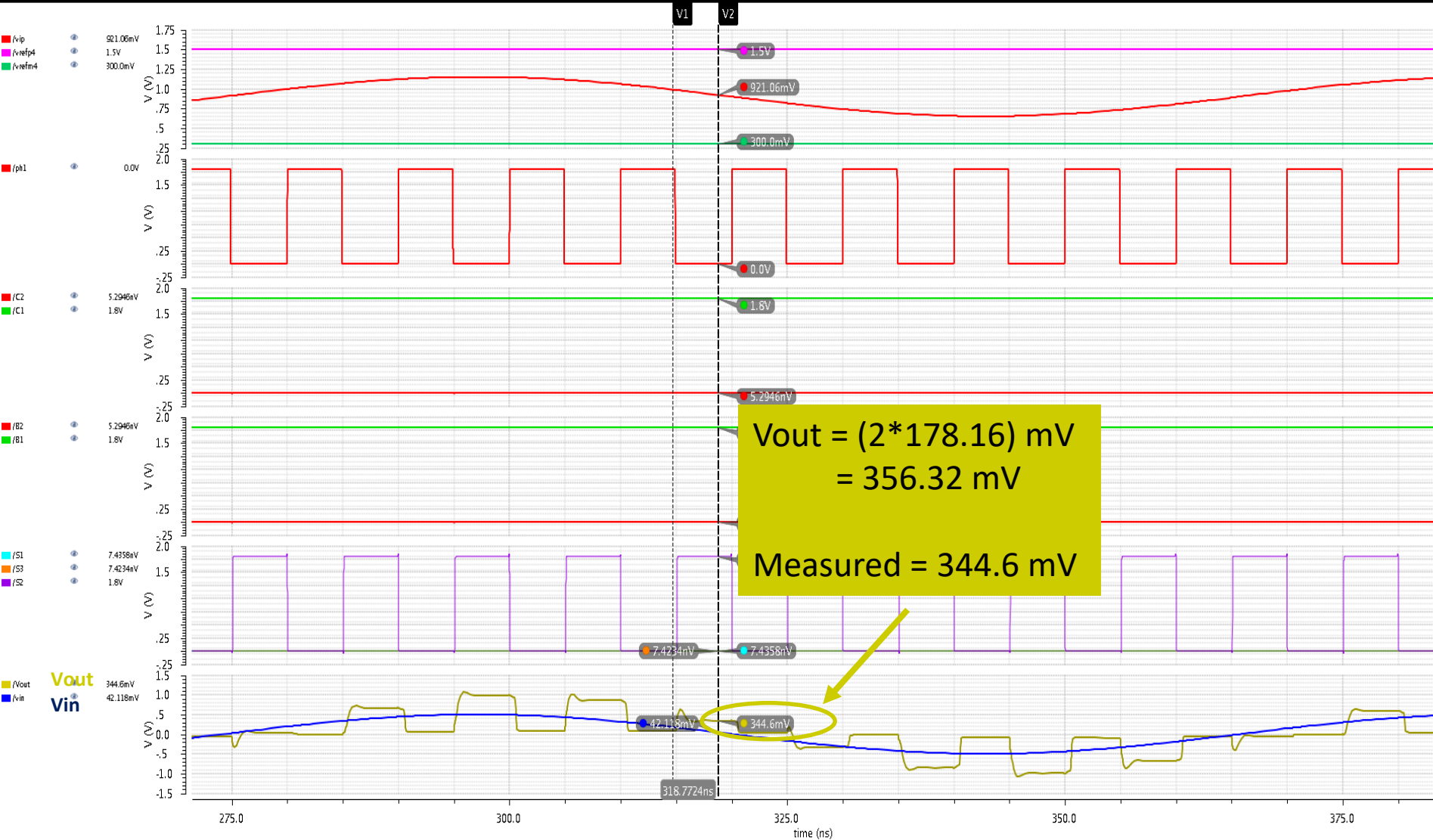


Simulation Results

2- 2x Gain Mode (Signal input Amp = 0.5v)

db20(dft(v("/Vout" ?result "tran") 59n 699.0n 64 "Rectangular"))

Name
■ spectrum_Vout
■ spectrum_Vout

DFT of
Output

 


Simulation Results

2- 2x Gain Mode (Signal input Amp = 0.25v)

Transient Response

Thu May 3 23:27:48 2018

 


Simulation Results

2- 2x Gain Mode (Signal input Amp = 0.25v)

Transient Response

Thu May 3 22:57:11 2018

 


Simulation Results

2- 2x Gain Mode (Signal input Amp = 0.25v)

Transient Response

Thu May 3 22:57:11 2018

 

Simulation Results


2- 2x Gain Mode (Signal input Amp = 0.25v)

db20(dft(v("/Vout" ?result "tran") 59n 699.0n 64 "Rectangular"))

Name
■ spectrum_Vout
■ spectrum_Vout

**DFT of
Output**

Measurement	Value
ENOB	9.7009201 (bits)
SINAD	60.162539 (dB)
SNR	60.162539 (dB)
SFDR	70.157958 (dB)
THD	0 (%)
Signal ...	-6.0243451 (dB)
DC Po...	-106.25167 (dB)
Noise F...	-81.238384 (dB)
Noise F...	-143.0387 (dB)

 


Simulation Results

2- 2x Gain Mode (Signal input Amp = 0.125v)

Transient Response

Thu May 3 23:09:44 2018

 


Simulation Results

2- 2x Gain Mode (Signal input Amp = 0.125v)

Transient Response

Thu May 3 23:09:44 2018

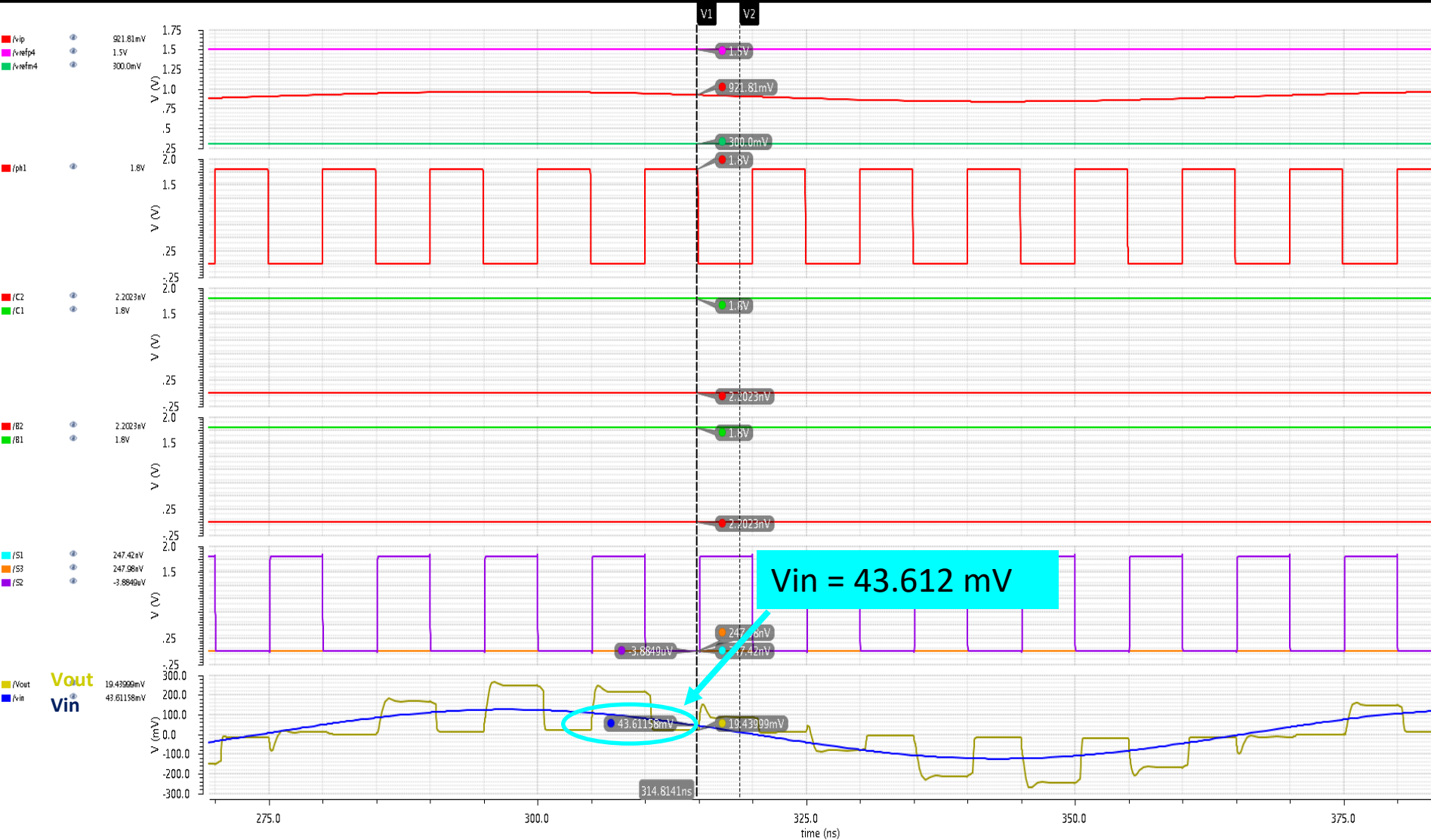


Simulation Results

2- 2x Gain Mode (Signal input Amp = 0.125v)

Transient Response

Thu May 3 23:09:44 2018

 

Simulation Results


2- 2x Gain Mode (Signal input Amp = 0.125v)

db20(dft(v("/Vout" ?result "tran") 59n 699.0n 64 "Rectangular"))

Name
■ spectrum_Vout
■ spectrum_Vout

**DFT of
Output**

Measurement	Value
v("/Vout" ?...	
... ENOB	8.8227454 (bits)
... SINAD	54.875928 (dB)
... SNR	54.875928 (dB)
... SFDR	66.392786 (dB)
... THD	0 (%)
... Signal ...	-12.039193 (dB)
... DC Po...	-111.5247 (dB)
... Noise F...	-81.966621 (dB)
... Noise F...	-143.76694 (dB)

 

Simulation Results

2- 2x Gain Mode

Input Amplitude	Difference between Ideal output value & Measured output value	ENOB	SNR
0.5 V	~ 12 mV	10.63 bits	65.76 dB
0.25 V	~ 2 mV	9.70 bits	8.82 dB
0.125 V	~ 1 mV	8.82 bits	54.88 dB

- It is observed that there is an offset between the measured 2x output with respect to the calculated value, & this offset decreases as the input signal amplitude decreases.
- As the amplitude of the input signal decreases, the signal power with respect to the noise decreases, causing a decrease in the ENOB & SNR values.

(5)

VerilogA Block

VerilogA:

1 stage 1.5 bit/stage ADC

```
// VerilogA for ADC_FinalProject, B_1p5stage_VerilogA, veriloga
```

```
`include "constants.vams"  
`include "disciplines.vams"
```

```
module B_1p5stage_VerilogA(vin,vrefp,vrefm,ph1,ph2,vcm,vout,D1,D0,vdd,vss);
```

```
parameter real clk_th=0.9;  
parameter real delay = 0;  
parameter real ttime = 1p;
```

```
inout vdd,vss;  
input vin,vrefp,vrefm,ph1,ph2,vcm;  
output vout,D1,D0;
```

```
electrical vdd,vss;  
electrical vin,vrefp,vrefm,ph1,ph2,vcm;  
electrical vout,D1,D0;
```

```
real dd1,dd0,vvout;
```


```
analog begin  
    @(cross(V(ph1) - clk_th, +1)) begin  
        if (V(vin)>V(vrefp)) begin  
            dd1 = V(vdd);    dd0 = V(vss);  
        end  
        else if ((V(vin)<V(vrefp)) && (V(vin)>V(vrefm))) begin  
            dd1 = V(vss);    dd0 = V(vdd);  
        end  
        else begin  
            dd1 = V(vss);    dd0 = V(vss);  
        end  
    end  
end
```

```
    @(cross(V(ph2) - clk_th, +1)) begin  
        if (dd1 > 0.9) begin  
            vvout = ((V(vin) - 0.9) * 2) - 1;  
        end  
        else if (dd0 > 0.9) begin  
            vvout = (V(vin) - 0.9) * 2;  
        end  
        else begin  
            vvout = ((V(vin) - 0.9) * 2) + 1;  
        end  
    end
```

```
V(D1) <+ transition(dd1,delay,ttime);  
V(D0) <+ transition(dd0,delay,ttime);  
V(vout) <+ transition(vvout,delay,ttime);
```

```
end  
endmodule
```


Testbench

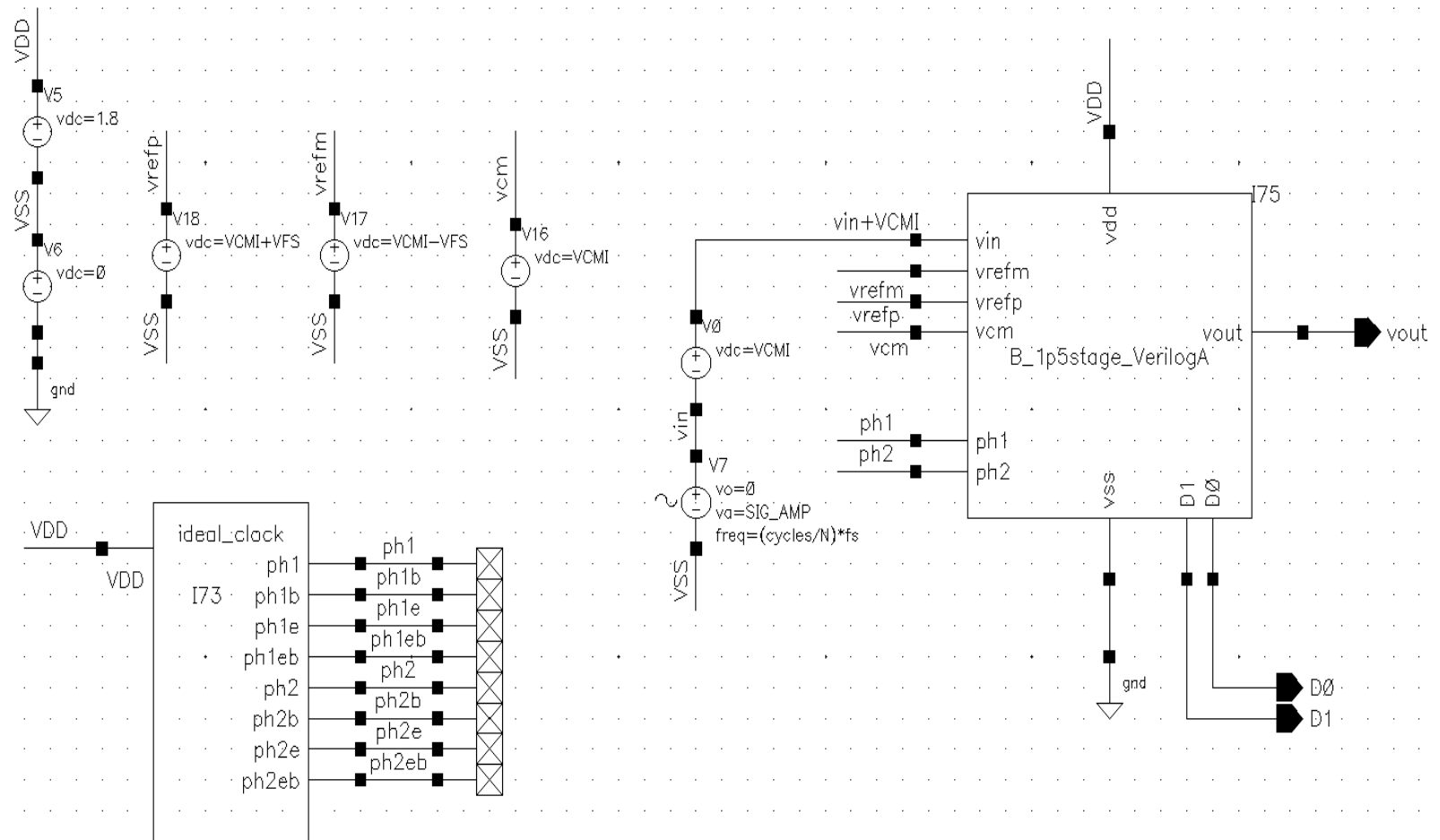


Simulation Results

1- Normal Mode

Transient Response

Sun May 6 17:49:07 2018

 


Simulation Results

1- Normal Mode

1) If $V_{in} < V_{refm}$ $\rightarrow V_{out} = 2 \cdot V_{in} + V_{fs}$

Transient Response

Sun May 6 17:49:07 2018

 


Simulation Results

1- Normal Mode

2) If $V_{refm} < V_{in} < V_{refp} \rightarrow V_{out} = 2 * V_{in}$

Transient Response

Sun May 6 17:49:07 2018

 


Simulation Results

1- Normal Mode

3) If $V_{in} > V_{refp}$ $\rightarrow V_{out} = 2 * V_{in} - V_{fs}$

Transient Response

Sun May 6 17:49:07 2018

 


Simulation Results

2- 2x Gain Mode

Transient Response

Sun May 6 18:07:44 2018

 


Simulation Results

2- 2x Gain Mode

Transient Response


Sun May 6 18:07:44 2018

 

Simulation Results

2- 2x Gain Mode

 db20(dft(v("vout") ?result "tran") 59n 699.0n 64 "Rectangular"))



[Extra] VerilogA: Sub-ADC Logic

```
// VerilogA for ADC_FinalProject, B_SubADCLogic, veriloga
```

```
`include "constants.vams"  
`include "disciplines.vams"
```

```
module B_SubADCLogic(C2,C1,ph2,S1,S2,S3,B2,B1,vdd,vss);
```

```
parameter real clk_th=0.9;  
parameter real delay = 0;  
parameter real ttime = 1p;
```

```
inout vdd,vss;  
input C2,C1,ph2;  
output S1,S2,S3,B2,B1;
```

```
electrical vdd,vss;  
electrical C2,C1,ph2;  
electrical S1,S2,S3,B2,B1;
```

```
real ss1,ss2,ss3,bb2,bb1;
```

```
analog begin
```

```
    @(cross(V(ph2) - clk_th, +1)) begin
```

```
        if ((V(C2)>0.9) && (V(C1)>0.9)) begin
```

```
            ss1 = V(vdd);    ss2 = V(vss);    ss3 = V(vss);
```

```
            bb2 = V(vdd);    bb1 = V(vss);
```

```
        end
```

```
        else if ((V(C2)<0.9) && (V(C1)>0.9)) begin
```

```
            ss1 = V(vss);    ss2 = V(vdd);    ss3 = V(vss);
```

```
            bb2 = V(vss);    bb1 = V(vdd);
```

```
        end
```

```
        else begin
```

```
            ss1 = V(vss);    ss2 = V(vss);    ss3 = V(vdd);
```

```
            bb2 = V(vss);    bb1 = V(vss);
```

```
        end
```

```
end
```

```
    @(cross(V(ph2) - clk_th, -1)) begin
```

```
        ss1 = V(vss);    ss2 = V(vss);    ss3 = V(vss);
```

```
    end
```

```
V(S1) <+ transition(ss1,delay,ttime);
```

```
V(S2) <+ transition(ss2,delay,ttime);
```

```
V(S3) <+ transition(ss3,delay,ttime);
```

```
V(B2) <+ transition(bb2,delay,ttime);
```

```
V(B1) <+ transition(bb1,delay,ttime);
```

```
end
```

```
endmodule
```

SUMMARY

Summary Notes:

- When replacing the ideal switches with switches with real transistors, for better performance, the CMOS transmission gate switches are preferably used to connect 2 nodes, while the Bootstrapped switches are used to pass exact input values to a certain node.
- The comparators compare the input signal at the rising edge of ph1, then the outputs are generated at the rising edge of ph2.
- The value of the stage output depends on the value of the input signal right before the falling edge of ph1 (rising edge of ph2).
- Decreasing the amplitude of the input signal, makes it easier for the system to give a more closer 2x gain (less offset), but also decreases the SNR & the ENOB (since the signal power decreased with respect to the noise level).