
EE288 Data Conversions/Analog Mixed-Signal ICs

Spring 2018

Revised Project Description

Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259

Remaining Schedule

4/25 Wed	Lecture on ADC OPAMP 2
4/30 Mon	Lecture on Oversampled ADC 1
5/2 Wed	Lecture on Oversampled ADC 2
5/7 Mon	HW6 Due and Review
5/9 Wed	Project Presentation 1
5/14 Mon	Project Presentation 2
5/21 Mon	Project Report Due

Revised Project Spec

▪ Process Technology	45nm CMOS with 0.18um I/O devices
▪ Process Corners	TT, FF, SS
▪ Supply Voltage	$V_{DD} = 1.8V \pm 5\%$
▪ Temperature Range	$0 \sim 70^{\circ}\text{C}$
▪ Sampling Rate, fs	50 MS/s
▪ Input Full Scale, VFS	1.6 Vppd
▪ Input Frequency	$(7/64) \cdot f_s$ MHz
▪ Power consumption	As small as possible
▪ 2x gain mode Linearity	10-bit ENOB at Typical, 7-bit at worst corner


Project Point Breakdown

Total point			40
Condition 1	Fully-Differential 1.5-bit Stage Design		10
		Typical corner (TT, 1.8V, 27C)	
		Vin = 0.8Vpp (Full scale signal)	
		fin = (cycles/N) * fs where cycles=7 and N=64	
		Fs = 50 MSPS	
		Real switches & Real opamp	
		ideal_clock, ideal_bias, and ideal voltages	
		Target: 10-bit ENOB at 2x gain mode with Vin=0.8Vpp	
		Report the results for Vin=0.4Vpp and 0.2Vpp as well	
Condition 2	Condition 1 plus	Worst case ENOB > 7-bit for 2x gain mode, Vin=0.8Vpp	10
		TT, 1.8V, 0C, 27C, 70C	
		TT, 27C, 1.7V, 1.8V, 1.9V	
		27C, 1.8V, TT, FF, SS	
		SS, 1.7V, 70C	
Presentation (5 min) on May 9 or 14			10
Project report in 4-page IEEE conference paper submission format (Due May 21)			10
Extra point		Functional Verilog-A codes for 10-bit ADC	5

Scoring Rule

- If your ENOB for TT corner is lower than 10-bit, you will get one point deduction for each ENOB you missed.
- If your ENOB for worst corner is lower than 7-bit, you will get one point deduction for each ENOB you missed.
- This rule will be applied to both the Presentation and the Report
 - For example, you have missed the target by 2-bit on Presentation day, but you missed the target by 1-bit on the final report, you will get a deduction of total 3-points.


1.5-Bit Stage Architecture

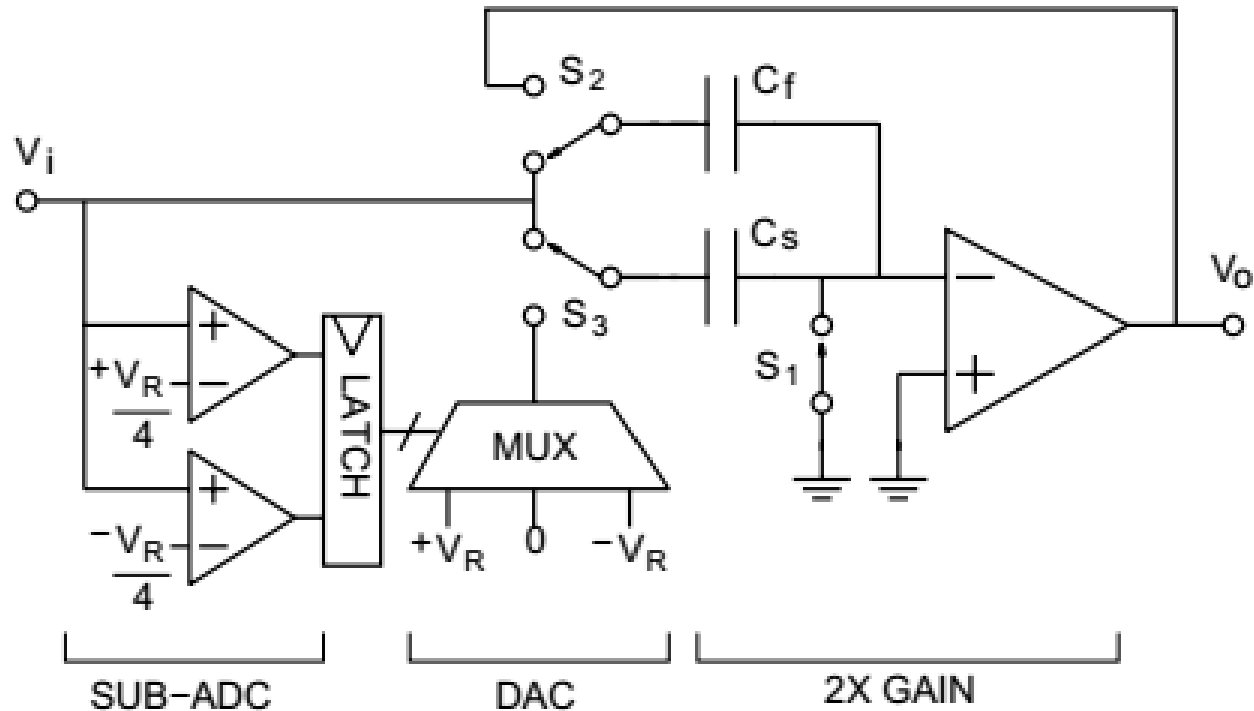

Reference Paper:


A. M. Abo and P. R. Gray, "A 1.5-V, 10-bit, 14.3-MS/s CMOS pipeline analog-to-digital converter," *IEEE J. Solid-State Circuits*, vol. 34, pp. 599–606, May 1999

1.5-Bit Stage Architecture

 

V_{IN}	Range	B1	B0	DAC O/P	Residue
$V_{IN} > V_H$	H	1	0	$+V_{REF}$	$2V_{IN} - V_{REF}$
$V_L < V_{IN} < V_H$	M	0	1	0	$2V_{IN}$
$V_H < V_L$	L	0	0	$-V_{REF}$	$2V_{IN} + V_{REF}$

Key Blocks To Design in the Project

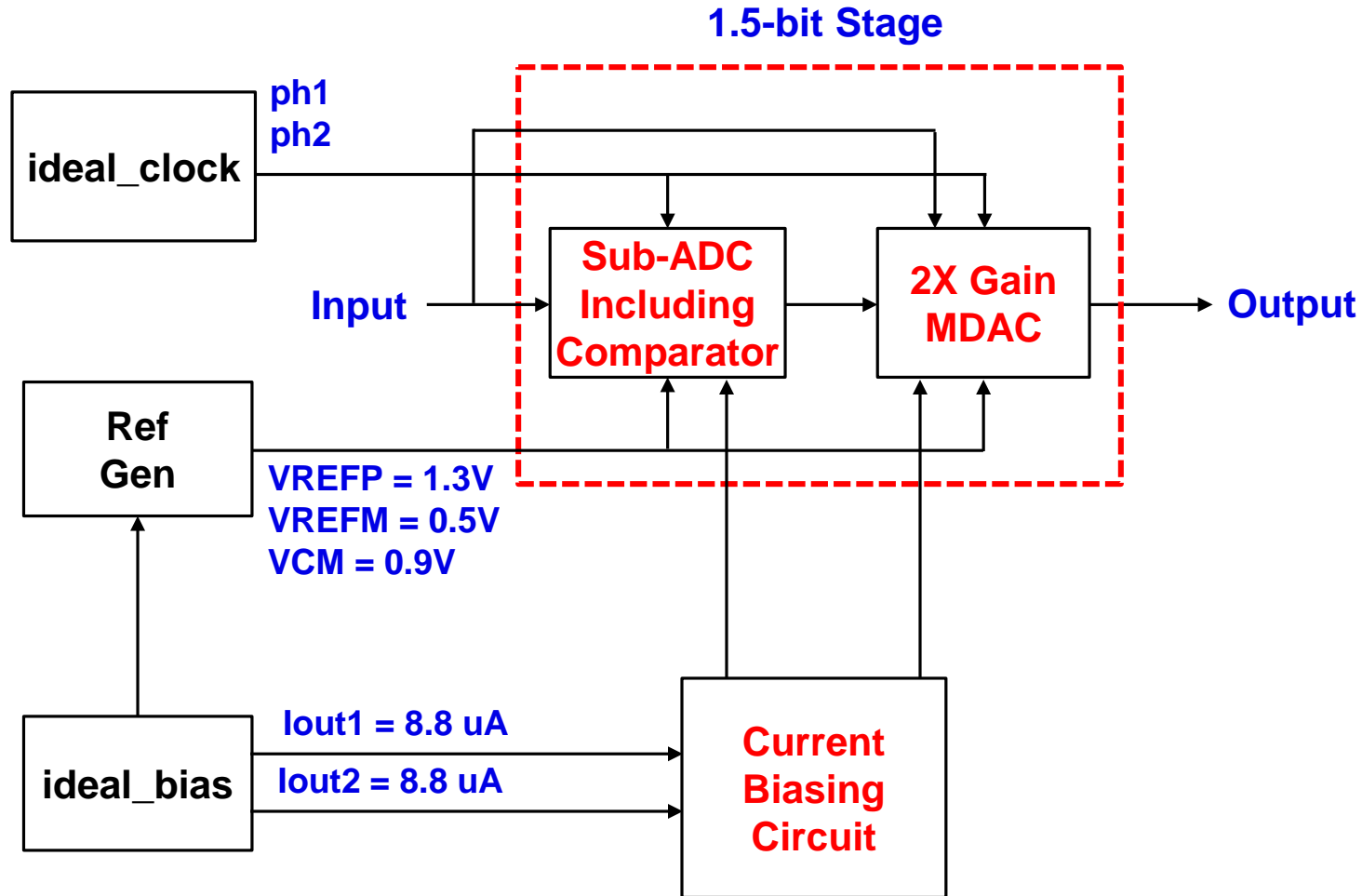

OPAMP Requirement


Resolution	Full Scale	Beta	Gain (dB)	Gain (dB)
N	V _{FS} (Volt)	β	$2 \cdot 2^N / (\beta \cdot V_{FS})$	20log(x)
10	0.8	1	5120	74
10	0.8	0.5	10240	80
11	0.8	1	10240	80
11	0.8	0.5	20480	86
12	0.8	1	20480	86
12	0.8	0.5	40960	92

Resolution	Full Scale	Beta	Sampling Rate	UGB
N	V _{FS} (Volt)	β	fs	fu
10	0.8	1	5.00E+07	1.25E+08
10	0.8	0.5	5.00E+07	2.50E+08
11	0.8	1	5.00E+07	1.36E+08
11	0.8	0.5	5.00E+07	2.72E+08
12	0.8	1	5.00E+07	1.47E+08
12	0.8	0.5	5.00E+07	2.94E+08

Implementation Detail

- Start with your HW6 design as a baseline
- Use **Ideal capacitor** cell “cap” from analogLib
- Use “**ideal_bias**” cell in ee288lib for master current sources
- Use “**ideal_clock**” cell in ee288lib for 2-phase non-overlapping clocks
- Use **Ideal DC voltage source** for all voltage references such as VREFP, VREFM, and VCM
- Assume **100fF loading capacitance** for your opamp
- You will need a switched-capacitor CMFB for your opamp

Differential Signal Swing

 

Items to prepare for project presentation

- Summary of your design
- Schematics
- Simulation Test Bench
- Simulation Results
 - OPAMP ac response
 - Comparator overdrive response
 - 1.5-bit Stage operation
 - 2x gain mode FFT plots for all 10 cases
 - Simulated average total power for the whole block (P)
 - TT case FoM calculation assuming the total ADC power = $10 \times P$

Presentation Logistics

- Total score for Project Presentation is 10 points
- You are required to send the presentation file to me by 5PM May 9
- If you miss this deadline, you will get 2-point deduction
- Your presentation time should be no more than 5 min
- If your presentation is over 7 min, you will get 2-point deduction for using longer time and be forced to stop at that point
- Presentation order will be decided on the presentation day by lottery
- 40% for Neatness and clearness of the presentation materials to check if the slides are done professionally or not
- 40% for block functionality to check if the individual block design is functional or not
- 20% on if you answered the questions correctly or not in the Q&A session following your presentation


Project Report Guideline

- Use the IEEE template file uploaded in project folder in Canvas
- Total report length should be 4-pages
- Report should include the following sections
 - Abstract
 - Introduction
 - Main sections
 - Conclusion
 - References


Project Report Score Breakdown

- Total score for Project Report is 10 point
- Project report due is May 21, Monday midnight – If you miss the due date, each additional day will be 5 point deduction
- 40% for Neatness and clearness to check if the report is done professionally and if the report follows IEEE format
- 40% for block functionality to check if the individual block design is functional or not
- 20% for full stage design functionality - If you are working with another student, both of you will get the same score for the report


Example OPAMP Circuits

 

[Ref. 1]

 

[Ref. 2]

 


[Ref. 3]

MDAC


MDAC 2X Gain

B_1	B_0	D_0	D_1	D_2
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	X	X	X

Sub-ADC to DAC Bit Logic

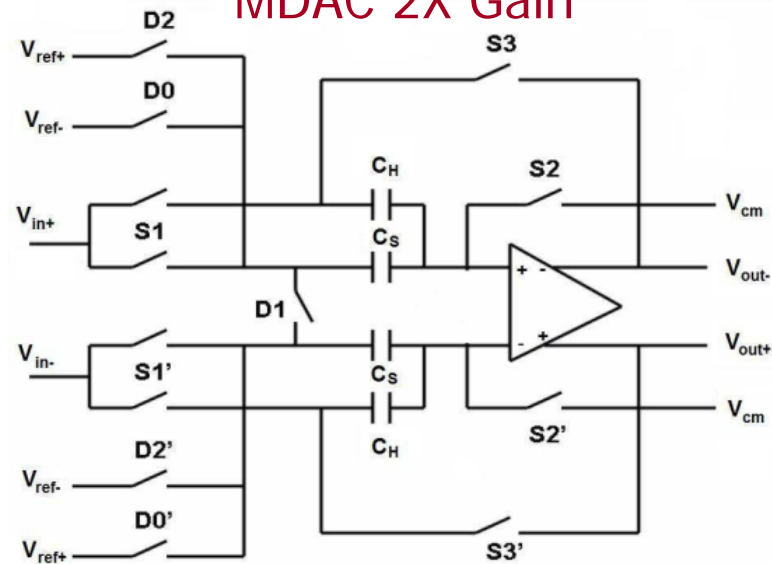

[Ref. 2]

 

References

1. A. M. Abo and P. R. Gray, "A 1.5-V, 10-bit, 14.3-MS/s CMOS pipeline analog-to-digital converter," *IEEE J. Solid-State Circuits*, vol. 34, pp. 599–606, May 1999
2. H. Ishii, K. Tanabe, and T. Iida, "A 1.0V 40mW 10b 100MS/s Pipeline ADC in 90nm CMOS," *IEEE Custom Integrated Circuits Conference*, pp. 10.5.1–10.5.4, 2005
3. M. Boulemlakher, "A 1.2V 4.5mW 10b 100MS/s Pipeline ADC in 65nm CMOS," *ISSCC*, pp. 250-251, 2008
4. M. E. Bayoumy, *MS Thesis, University of Texas, Austin*, A Study of 10-bit, 100Msps Pipeline ADC and the Implementation of 1.5-bit Stage, 2013
5. Overview of Pipelined ADC Chapter 13 from the book by M. Figueiredo et al., *Reference-Free CMOS Pipeline Analog-to-Digital Converters*, 2013