

VerilogA Blocks  
For a 10-bit Pipelined ADC


# VerilogA:

## 1 stage 1.5 bit/stage ADC

```
// VerilogA for EE288, One_stage_pipeline_ADC, veriloga
`include "constants.vams"
`include "disciplines.vams"
module One_stage_pipeline_ADC(vdd,vss, vin,vrefm,vrefp,out,ph1,ph2,b0,b1,vcm);
input vrefm,vrefp,ph1,ph2,vcm,vin;
inout vss,vdd;
output out,b0,b1;
electrical vin,out,vss,vdd,vrefm,vrefp,ph1,ph2,b0,b1,vcm;
parameter real clk_vth = 0.5, delay = 0, ttime = 1p;
real v,B0,B1, vp, vm, vinput;
analog begin
vp = V(vcm) + (V(vrefp)-V(vrefm))/8;
vm = V(vcm) - (V(vrefp)-V(vrefm))/8;
@(cross(V(ph1) - clk_vth,-1)) begin
    if((V(vin) >= vp))
        begin
            B0 = V(vss);
            B1 = V(vdd);
        end
    else if ((V(vin)<= vp ) && (V(vin)>= vm)) begin
        B0 = V(vdd);
        B1 = V(vss);
    end
    else begin
        B0 = V(vss);
        B1 = V(vss);
    end
end
end
```

```
@(cross(V(ph2) - clk_vth,+1)) begin
    if((B1 >= 0.9)) begin
        v = (V(vin)*2) - V(vrefp);
    end
    else if((B0 >= 0.9)) begin
        v = (V(vin)*2) - V(vcm);
    end
    else begin
        v = (V(vin)*2) - V(vrefm);
    end
end
V(out) <+ transition(v,delay,ttime);
V(b0) <+ transition(B0,delay,ttime);
V(b1) <+ transition(B1,delay,ttime);
endendmodule
```

# Testbench

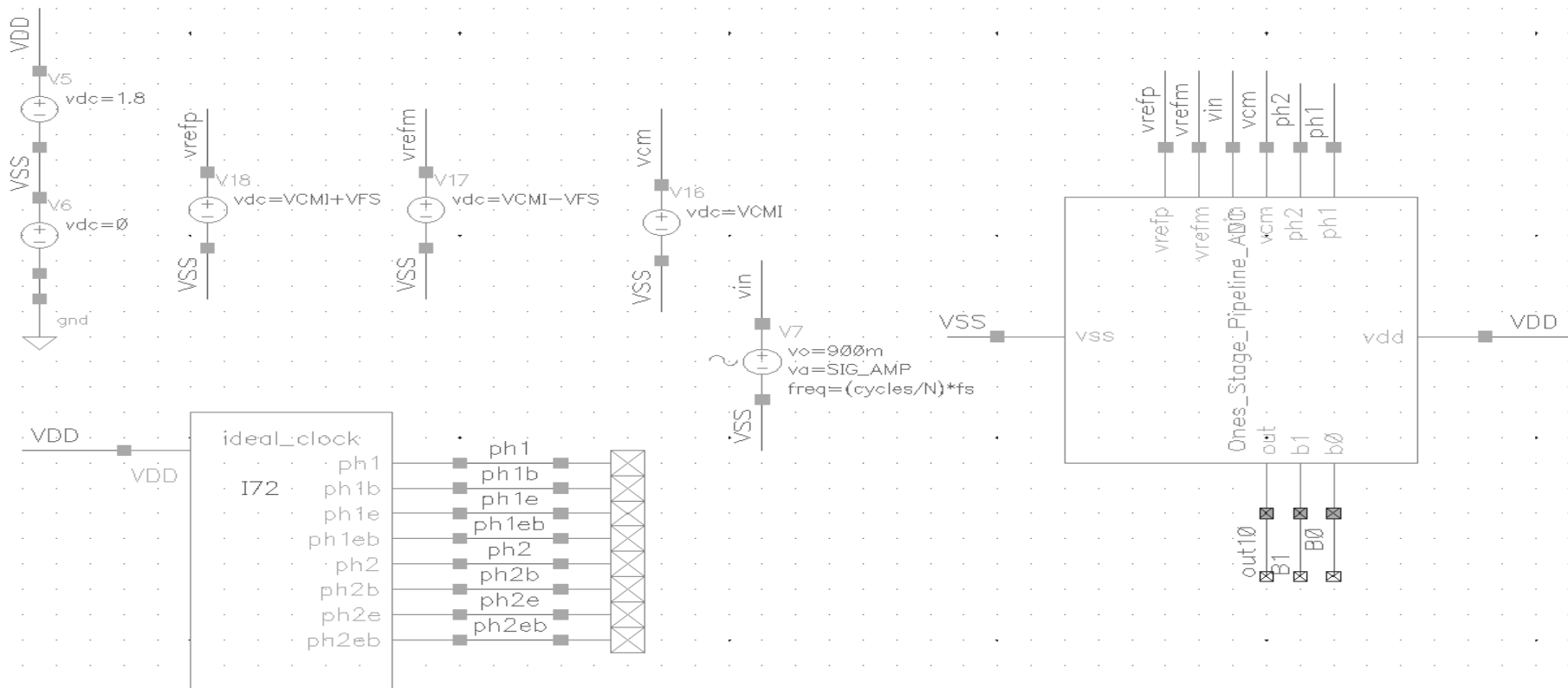


# Simulation Results

## 1- Normal Mode

- 1) If  $V_{in} < V_{refm} \rightarrow V_{out} = 2 \cdot V_{in} + V_{fs}$


Transient Response

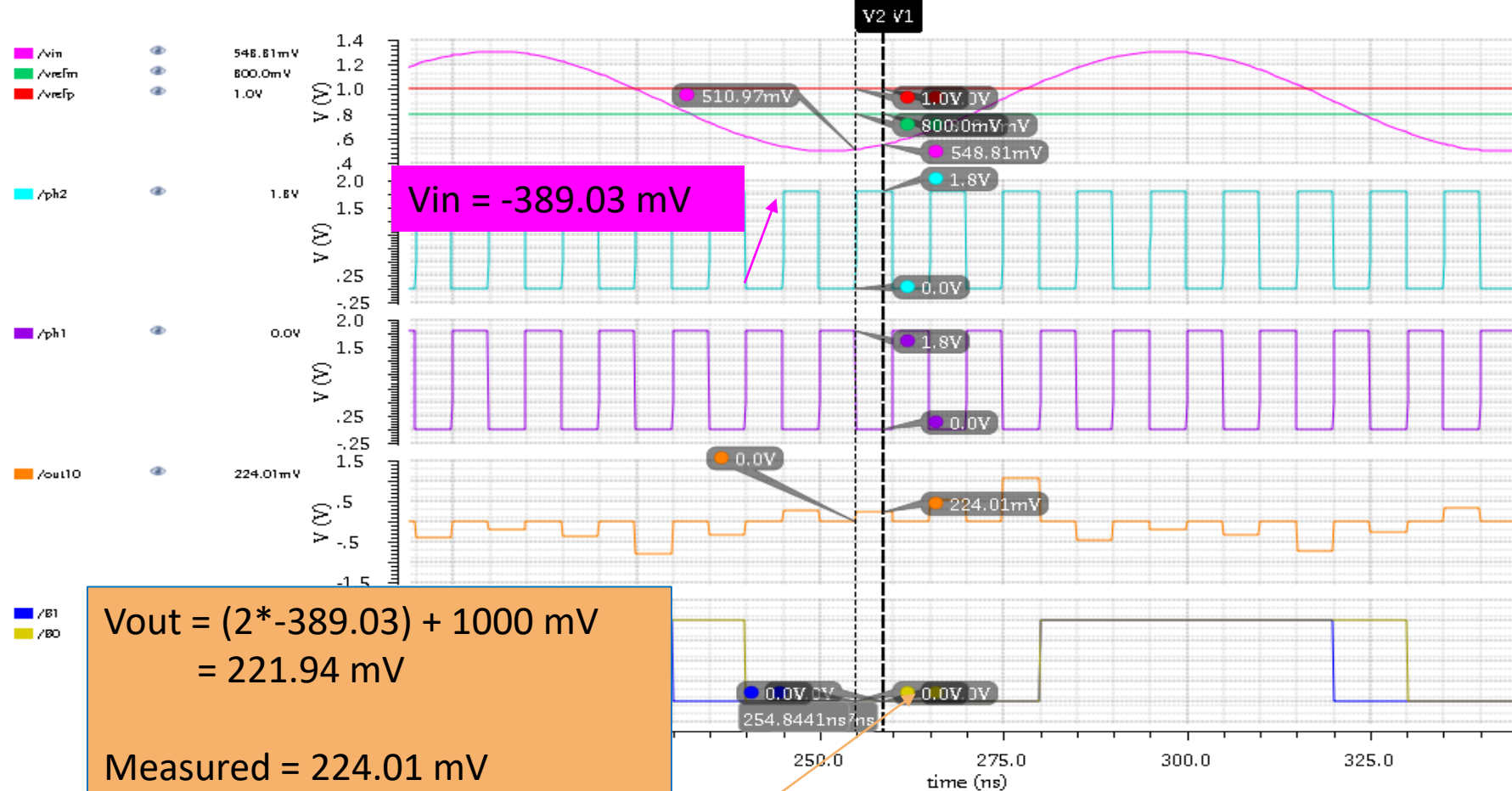

# Simulation Results

## 1- Normal Mode

 2) If  $V_{refm} < V_{in} < V_{refp} \rightarrow V_{out} = 2 * V_{in}$




# Simulation Results

## 1- Normal Mode

3) If  $V_{in} > V_{refp} \rightarrow V_{out} = 2 \cdot V_{in} - V_{fs}$

$V_{in} = 399.4 \text{ mV}$

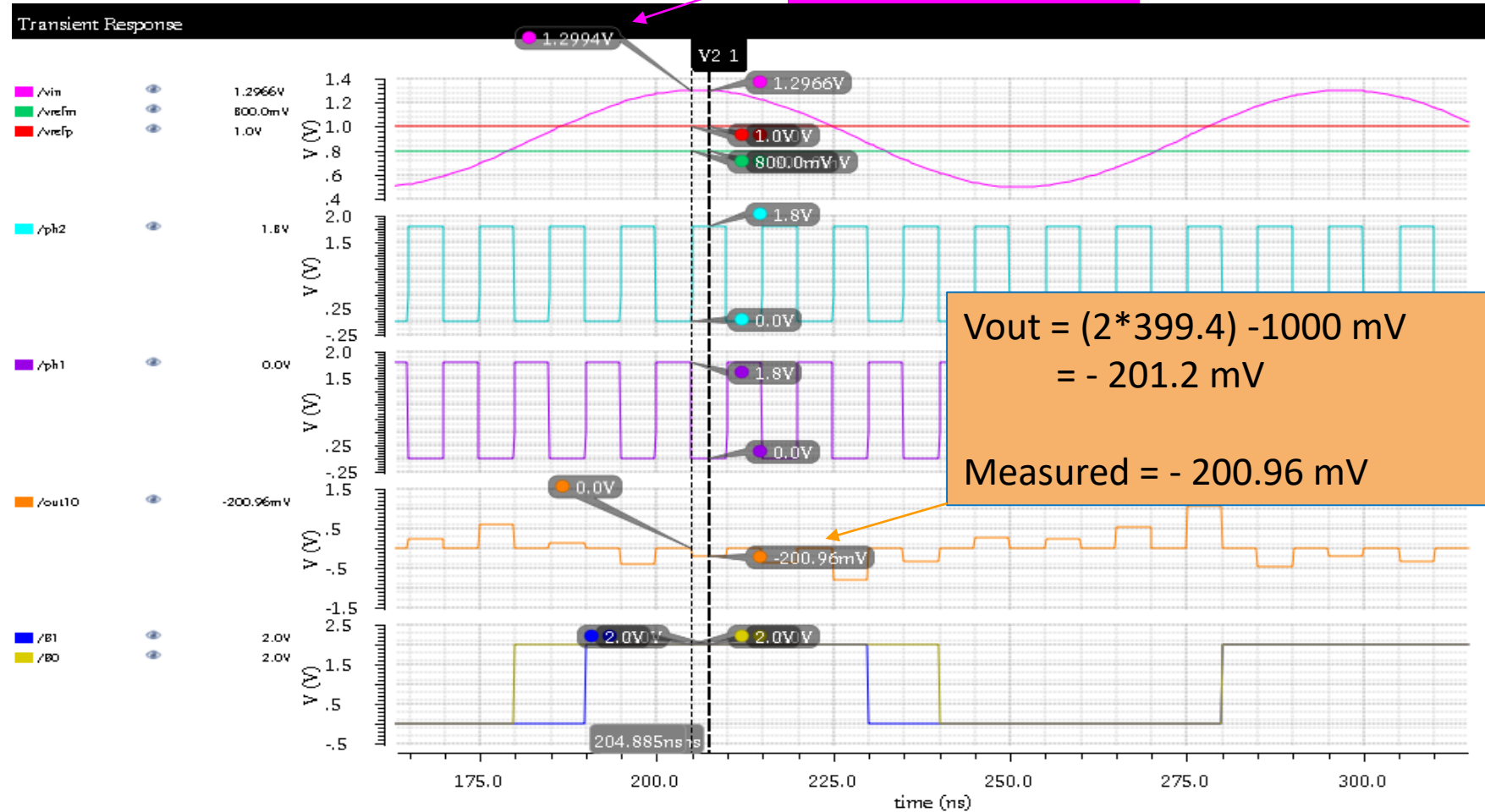


$$V_{out} = (2 \cdot 399.4) - 1000 \text{ mV} \\ = -201.2 \text{ mV}$$

Measured = -200.96 mV

# Simulation Results

## 2- 2x Gain Mode

Transient Response

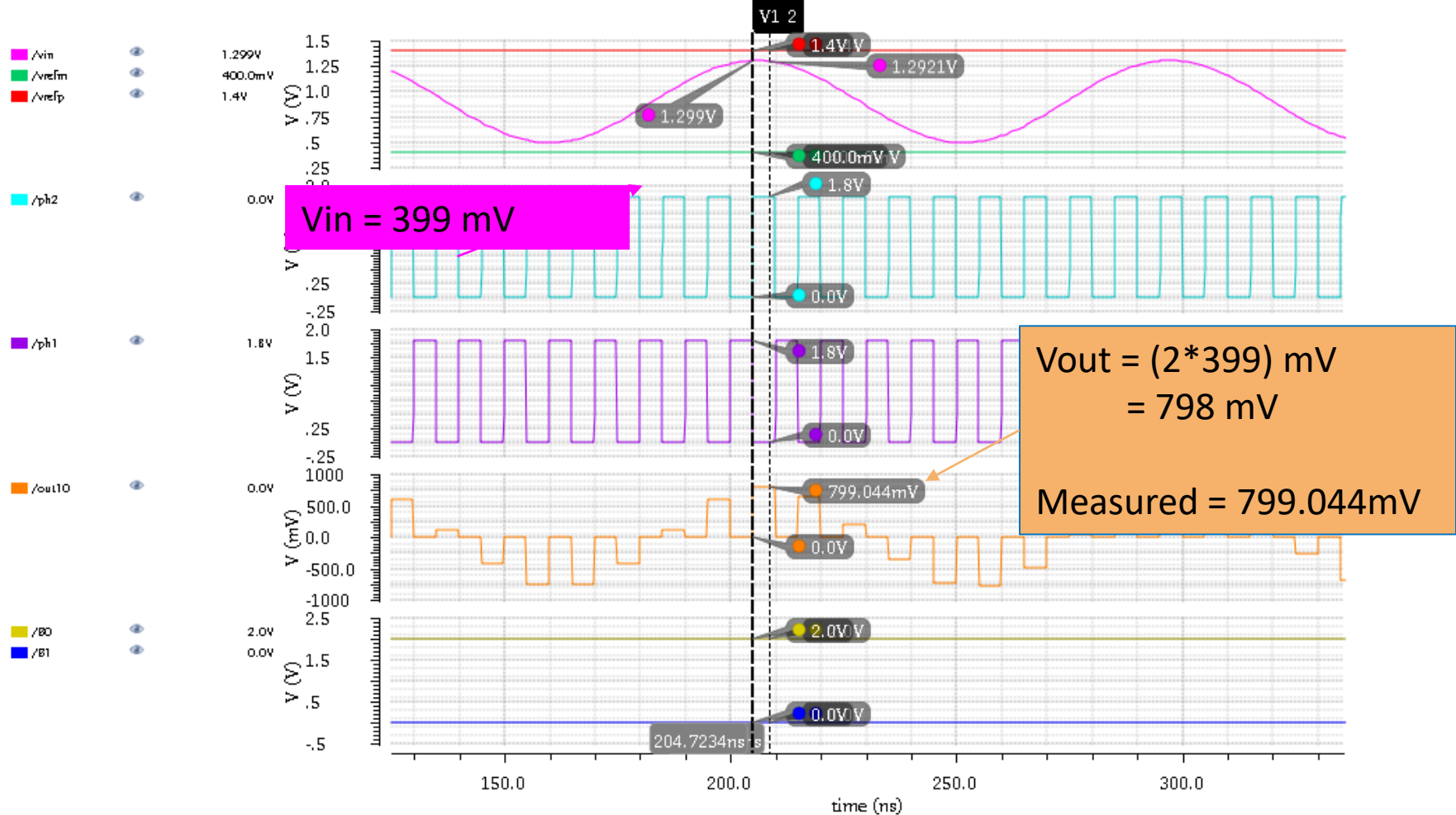

# VerilogA: Half Adder

```
// VerilogA for EE288, half_adder, veriloga
```

```
`include "constants.vams"  
`include "disciplines.vams"
```

```
module half_adder(A,B,Cout,VDD,VSS,S );
```

```
input A, B;
```

```
output Cout,S;
```

```
inout VDD, VSS;  
parameter real delay = 0, ttime = 1p;  
real carri, sum;
```

```
electrical A, B, Cout, S, VSS, VDD;
```

```
analog begin
```

```
if( (V(A)>=0.5) && (V(B)>=0.5) ) begin
```

```
    carri = V(VDD);
```

```
end
```

```
else begin
```

```
    carri = V(VSS);
```

```
end
```

```
if( (((V(A)>=0.5) && (V(B)>=0.5)) || ((V(A)<=0.5) && (V(B)<=0.5)))) begin
```

```
    sum = V(VSS) ;
```

```
end
```

```
else begin
```

```
    sum = V(VDD);
```

```
end
```

```
V(Cout) <+ transition(carri,delay,ttime);
```


```
V(S) <+ transition(sum,delay,ttime);
```

```
end
```


```
endmodule
```



# Testbench

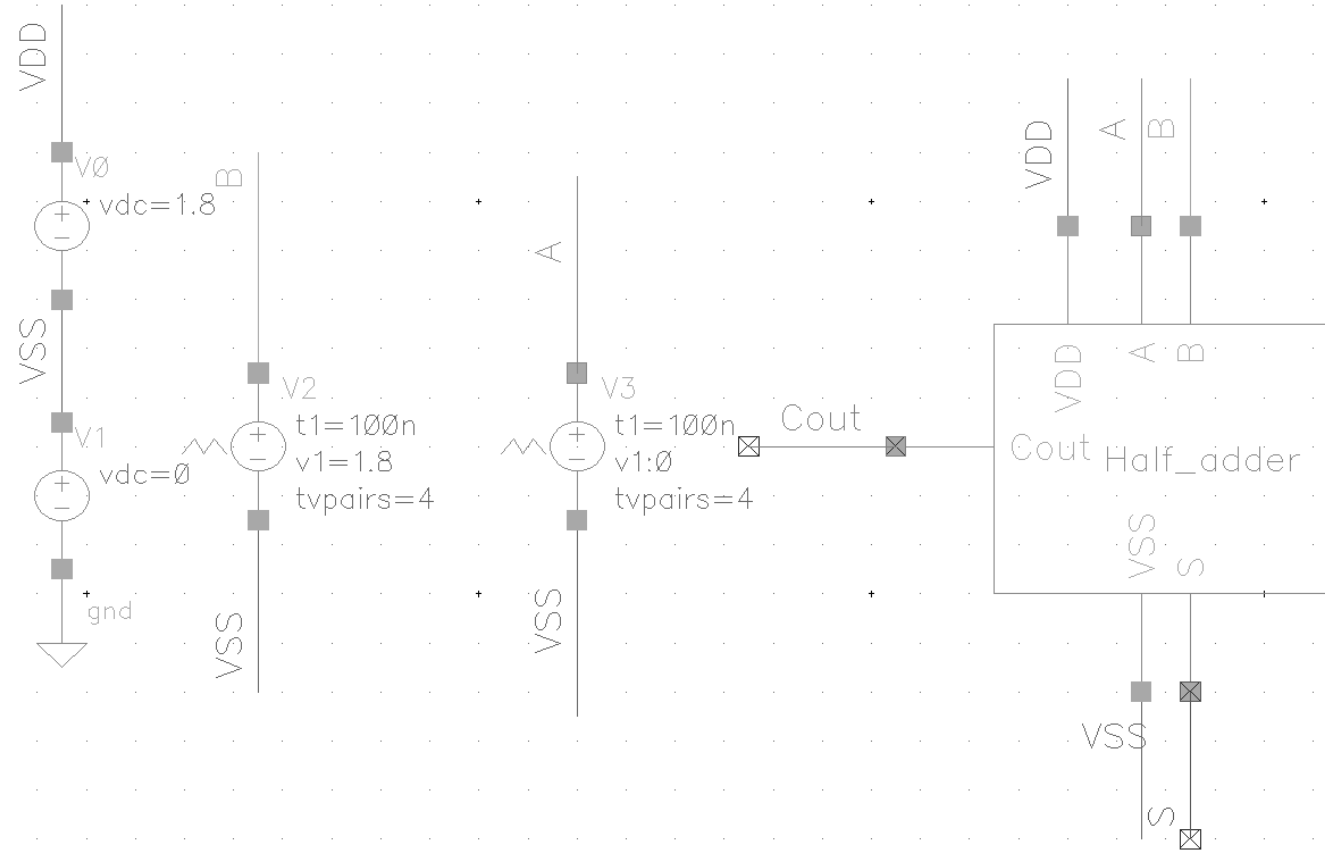

# Simulation Results

 


# VerilogA: Full Adder


```
// VerilogA for EE288, Full_Adder, veriloga
`include "constants.vams"
`include "disciplines.vams"
module Full_Adder(A,B,Cout,VDD,VSS,S,Cin );
input A, B,Cin;
output Cout,S;
inout VDD, VSS;
parameter real delay = 0, ttime = 1p;
real carri, sum,xor1,AND1,AND2;
electrical A, B, Cout, S, VSS, VDD,Cin;
analog begin
    if( ((V(A)>=0.9 && (V(B)>=0.9)) || (V(A)<=0.5 && (V(B)<=0.5)))) begin
        xor1=V(VSS);
    end
    else begin
        xor1 = V(VDD);
    end
    if( ((V(Cin)>=0.9 && (xor1>=0.9)) || (V(Cin)<=0.5 && (xor1<=0.5)))) begin
        sum= V(VSS);
    end
    else begin
        sum = V(VDD);
    end
end
```

```
if( (V(A)>=0.9) && (V(B)>=0.9) ) begin
    AND1 = V(VDD);
end
else begin
    AND1 = V(VSS);
end
if( (xor1>=0.9) && (V(Cin)>=0.9) ) begin
    AND2 = V(VDD);
end
else begin
    AND2 = V(VSS);
end
if((AND1 >= 0.9) || (AND2 >= 0.9) ) begin
    carri= V(VDD);
end
else begin
    carri = V(VSS);
end
V(Cout) <+ transition(carri,delay,ttime);
V(S) <+ transition(sum,delay,ttime);
end
endmodule
```

# Testbench

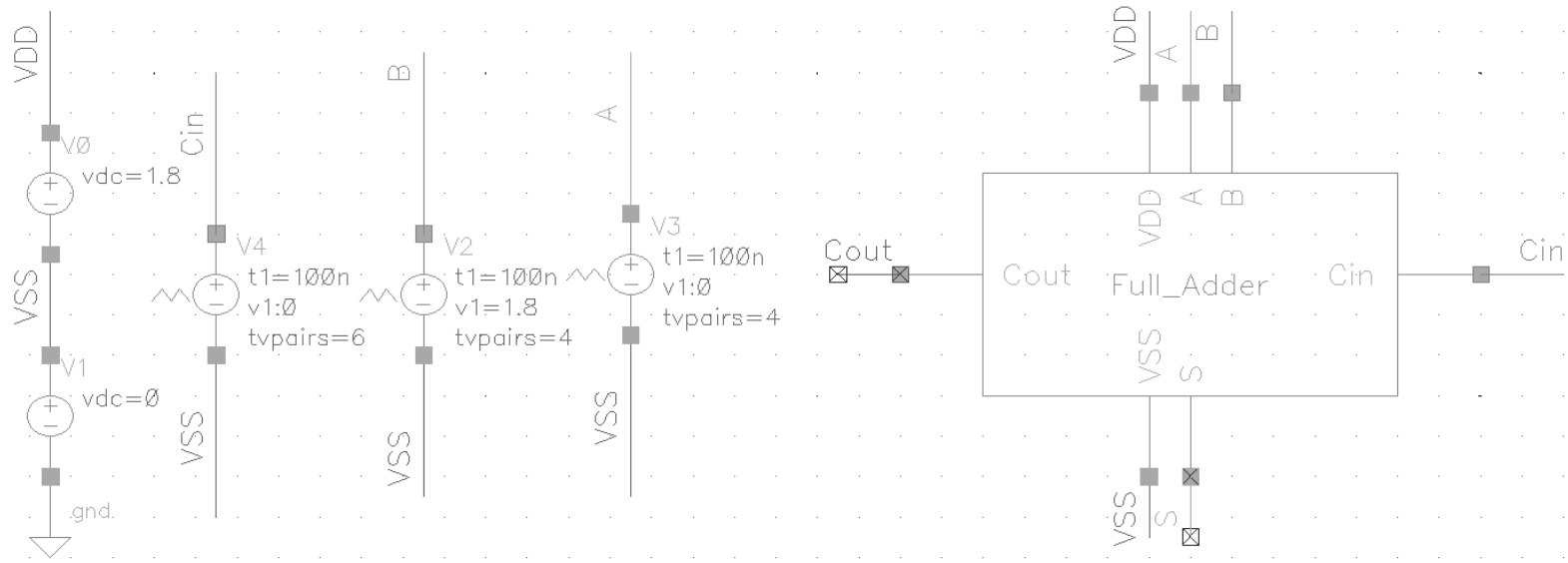

# Simulation Results

 

# VerilogA: D flipflop

```
// VerilogA for EE288, D_Flip_Flop, veriloga
`include "constants.vams"
`include "disciplines.vams"

module D_Flip_Flop(D,CLK,Q);

input D, CLK;
output Q;


parameter real clk_vth = 0.5, delay = 0, ttime = 1p;
real out;
electrical D, CLK, Q;

analog begin


    @(cross(V(CLK) - clk_vth,+1)) begin
        out = V(D);
    end
    V(Q) <+ transition(out,delay,ttime);

end
endmodule
```

# Testbench

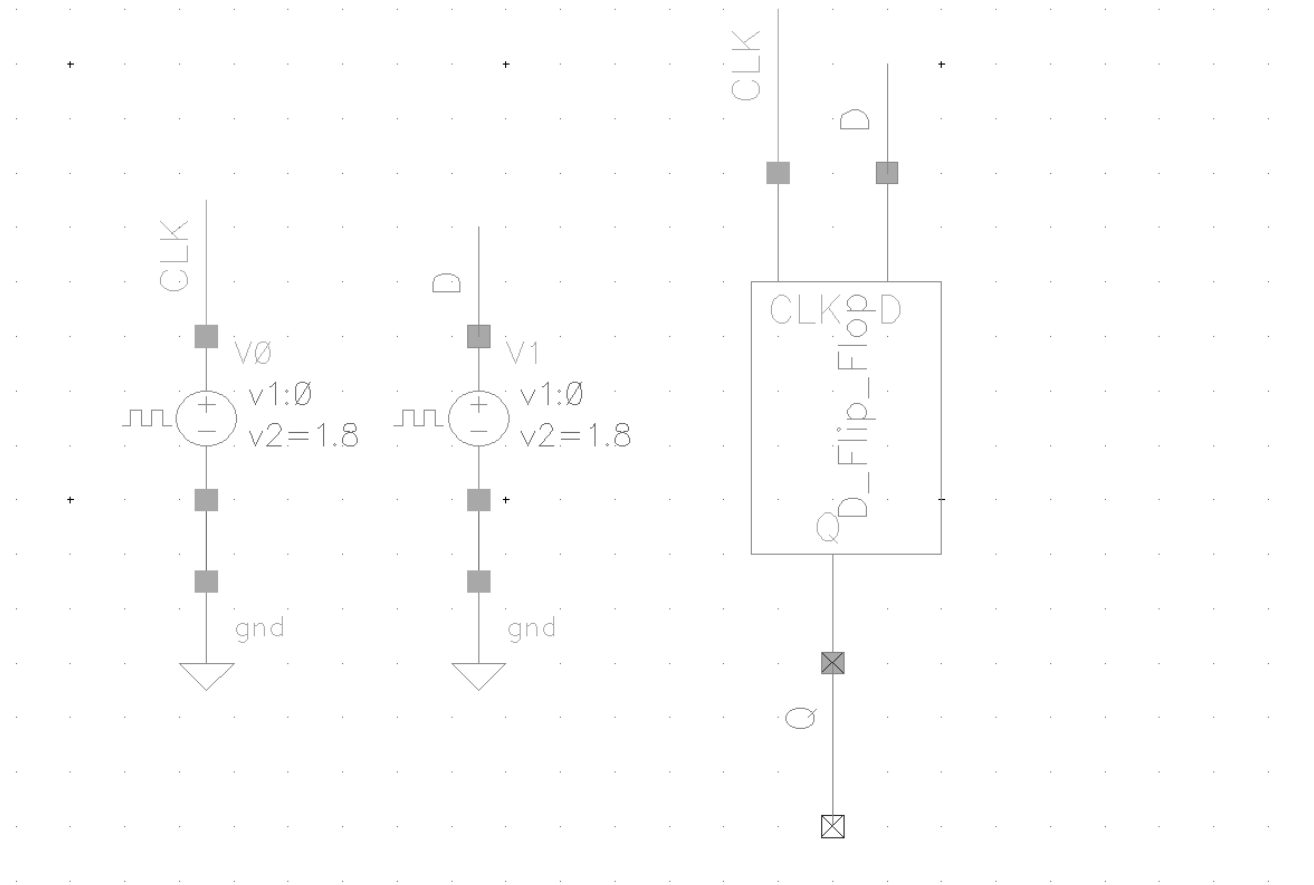

# Simulation Results

 



# VerilogA:

## Two Bit Flash ADC

```
// VerilogA for ADC_Comparator, Two_Bit_Flash_ADC, veriloga
`include "constants.vams"
`include "disciplines.vams"
module Two_Bit_Flash_ADC(ph1, ph2, Vrefp, Vrefm, Vin, VDD, D0, D1 );

input ph1, ph2, Vrefp, Vrefm, Vin;
inout VDD;
output D0, D1;
electrical ph1, ph2, Vrefp, Vrefm, Vin, VDD, D0, D1 ;
parameter real clk_th = 0.5, delay=0, ttime = 1p;

real c1, c2, c3, d1, d0;

analog begin


    @(cross(V(ph1) - clk_th, +1)) begin

        if ((V(Vin)) > (V(Vrefp)-V(Vrefm))/2) begin
            c2 = V(VDD);
            c1 = V(VDD);
            c3 = V(VDD);
            d1 = 0;
            d0 = 0;
        end
    else begin
```


```
        if ((V(Vin)) > (V(Vrefp)-V(Vrefm))/4) begin
            c3 = 0;
            c2 = V(VDD);
            c1 = V(VDD);
            d1 = 0;
            d0 = 0;
        end
        if ((V(Vin)) > (V(Vrefp)-V(Vrefm))/8) begin
            c3 = 0;
            c2 = 0;
            c1 = V(VDD);
            d1 = 0;
            d0 = 0;
        end
    else begin
        c3 = 0;
        c2 = 0;
        c1 = 0;
        d1 = 0;
        d0 = 0;
    end
end
enD
@(cross(V(ph2) - clk_th, +1)) begin
    if(c3 >= V(VDD)) begin
        d1 = V(VDD);
        d0 = V(VDD);
    end
```

```
    else begin
        if(c2 >= V(VDD)) begin
            d1 = V(VDD);
            d0 = 0;
        end
    else begin
        if (c1 >= V(VDD)) begin
            d1 = 0;
            d0 = V(VDD);
        end
    else begin
        d1 = 0;
        d0 = 0;
    end
    end
end
V(D0) <+ transition(d0, delay, ttime);
V(D1) <+ transition(d1, delay, ttime);
end
endmodule
```


# Testbench

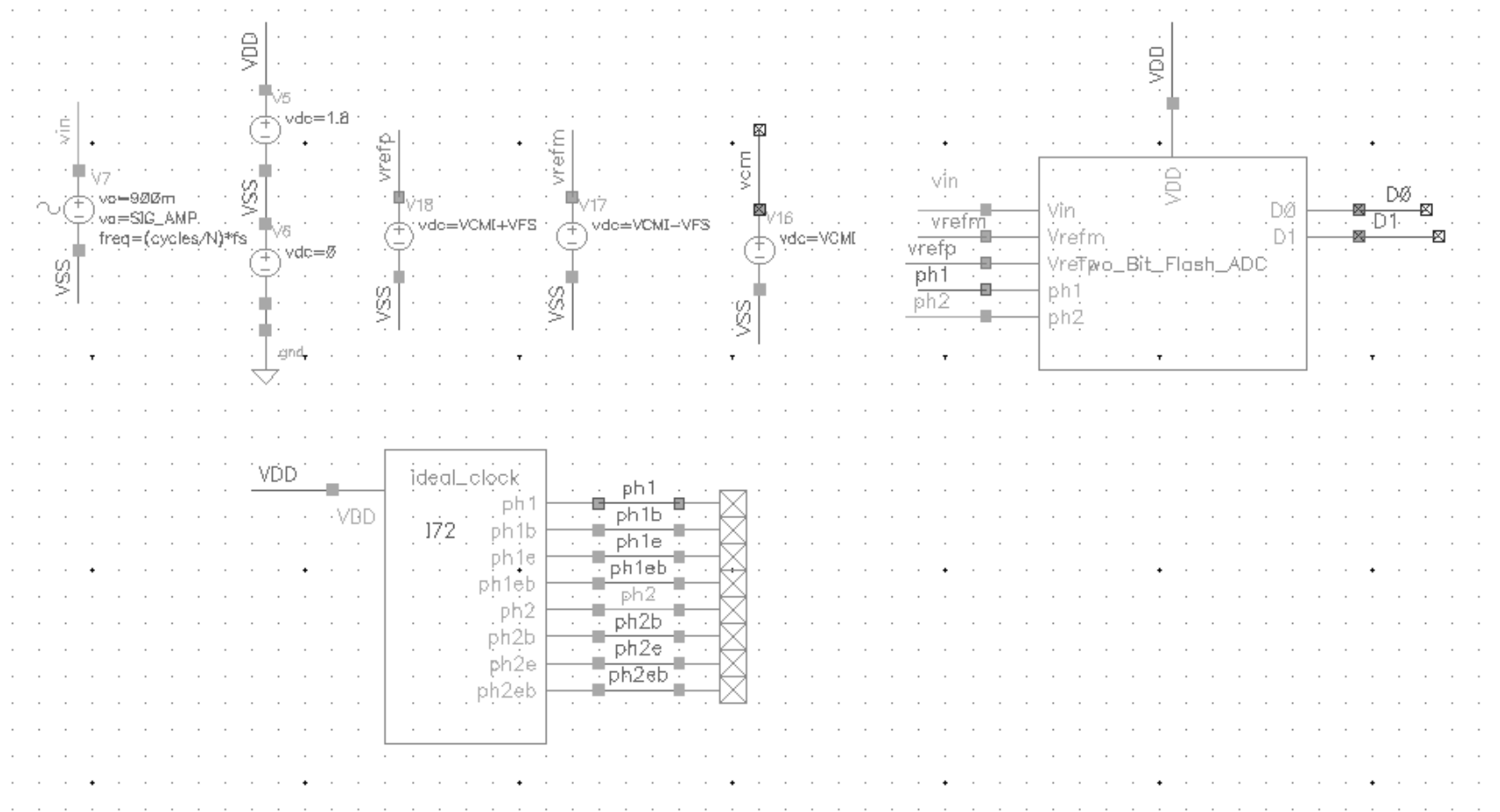


# Simulation Results

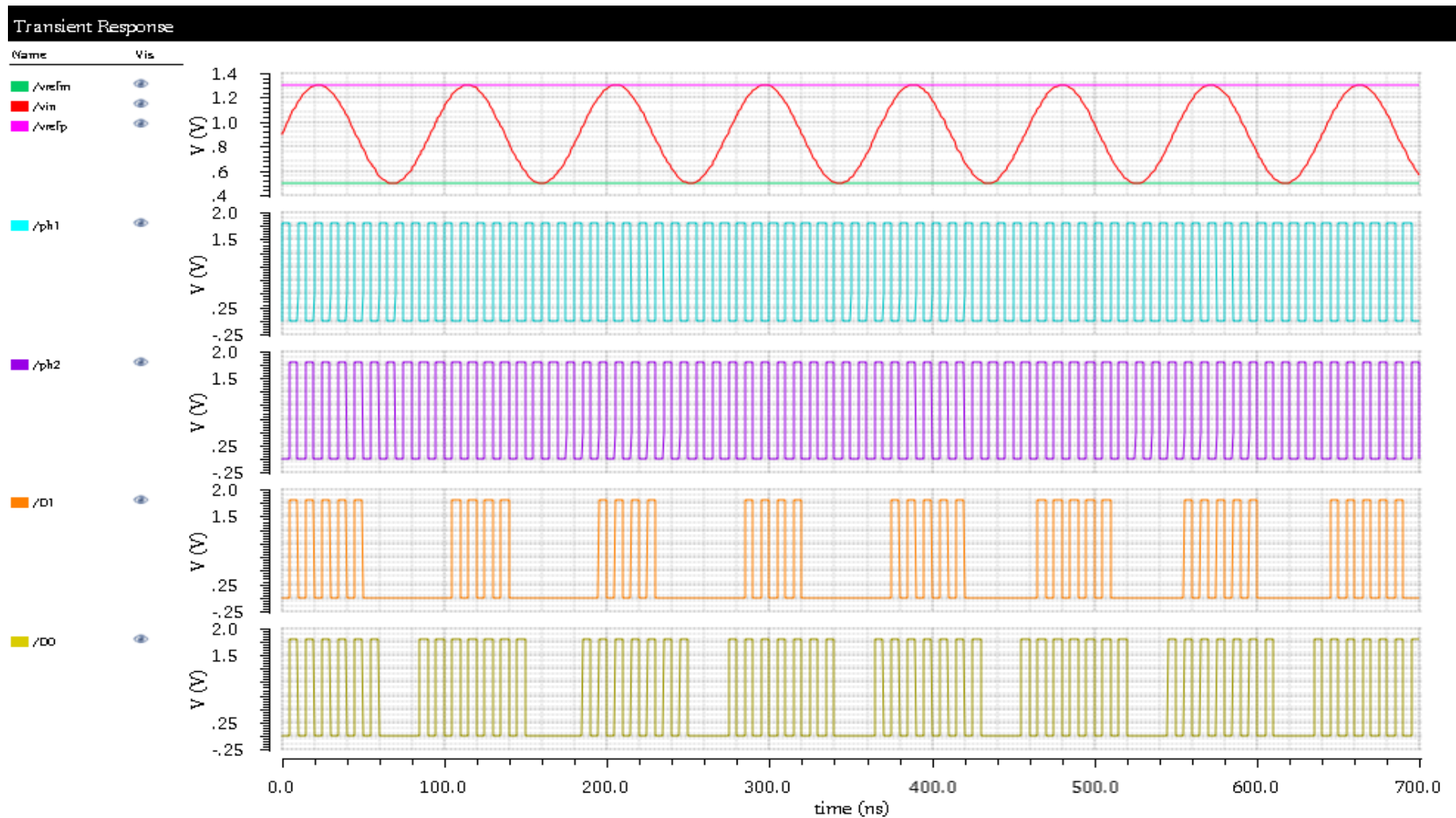


# Bit Alignment Circuit

 


# 10 Bit Pipe-Line ADC Test Bench

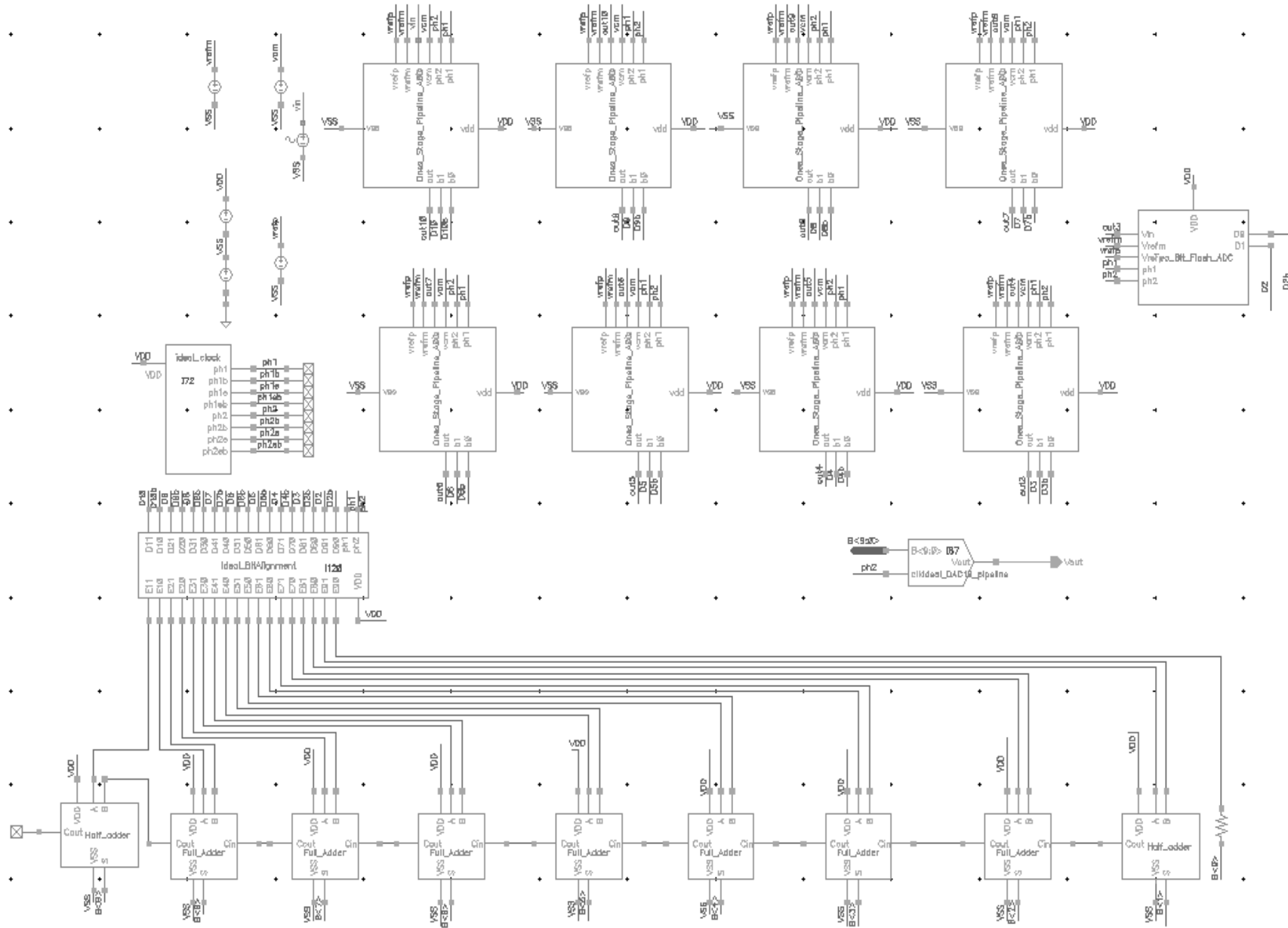


# Transient Response

 

# Transient Response

 

# FFT

 

### Spectrum

Signal/Expr Names

Vout

Input wave type: Time Domain Waveform

FFT Input method: Calculate Sample Frequency

Start/Stop Time: 109n 749n

Sample Count/Freq: 64 100.0M

Window Type: Rectangular

Plot FFT (Units): ☒ dB

Start/End Freq: 1.563M:50.00M

Signal bins: 0

Peak Sat. Level: 0.0

Harmonics: 1

Analysis Type: Signal Analysis

Plot Mode: New Subwindow

Plot

### Outputs

Measurement	Value
Vout	
ENOB	8.6487803 (bits)
SINAD	53.828658 (dB)
SNR	53.828658 (dB)
SFDR	61.207841 (dB)
THD	0 (%)
Signal ...	-0.91614038 (dB)
DC Po...	-0.89926002 (dB)
Noise F...	-69.796298 (dB)
Noise F...	-131.59662 (dB)